

ENGR 210 / CSCI B441
“Digital Design”

SPI I

Andrew Lukefahr

Announcements

- P8 – Elevator Controller is out
 - This one is hard.
- P9 – SPI is out
 - This one is new. Might be some changes.
- The end is in sight...

`for (; ;)` Loops in Verilog

- Testbenches – just like C/C++
- Synthesizable modules - more like `#define`

Always specify
defaults for
always_comb!


BLOCKING (=) FOR
`always_comb`

NON-BLOCKING (<=) for
`always_ff`


Lock State Machine



- Recall: 5 - 4 - 3
- E: relock

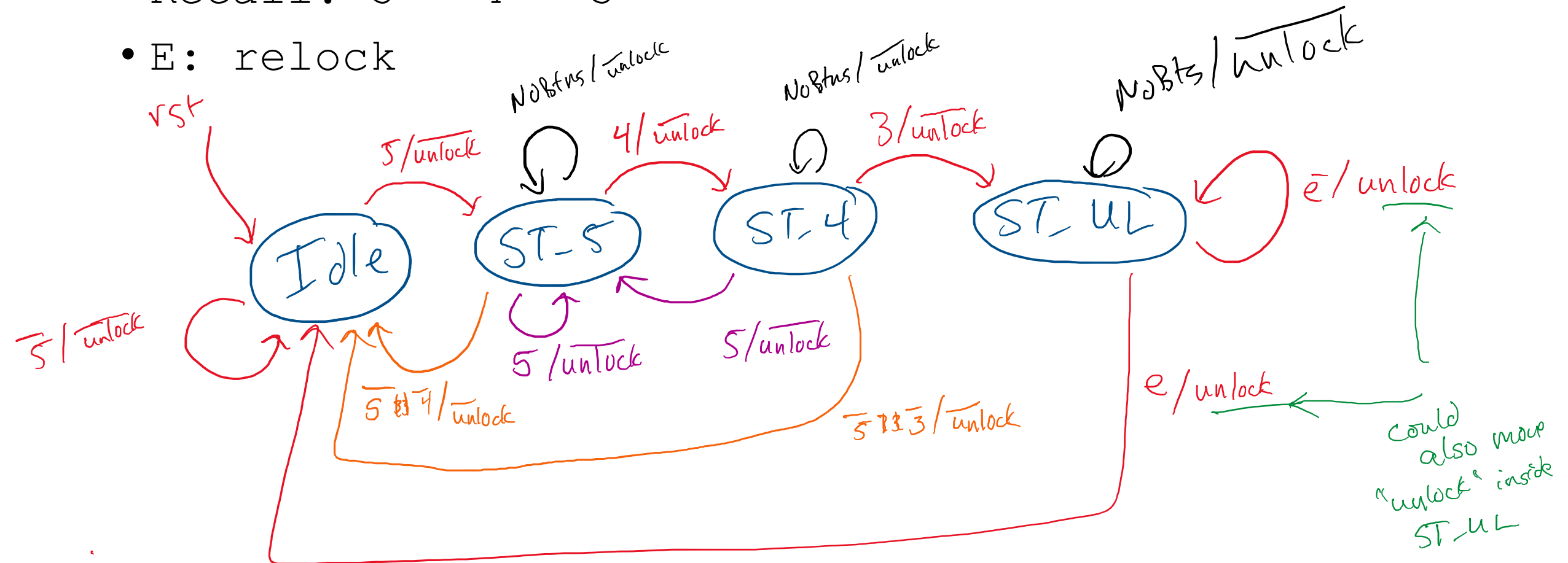

State Machine in Verilog

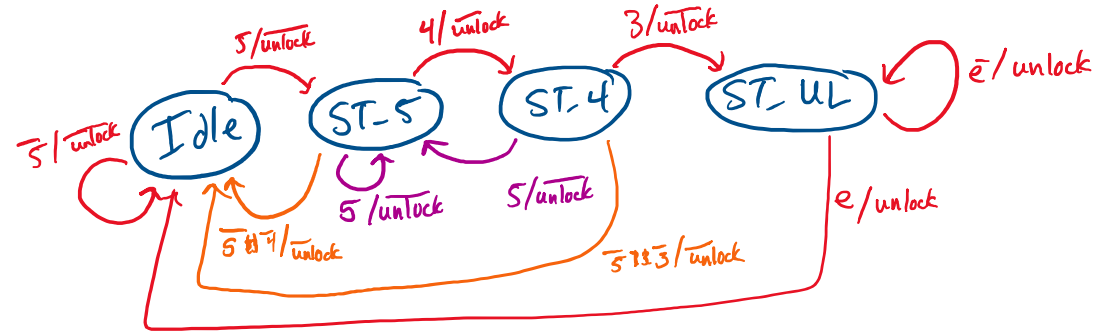

```
module Lock(
    input clk, rst,
    input [9:0] num,
    input e, //relock
    output unlock
);
```

```
enum {ST_IDLE, ST_5, ST_4, ST_UL } state, next_state;
```


```
//seq logic
always_ff @(posedge clk) begin
    if (rst) state <= ST_IDLE;
    else      state <= next_state;
end
```

State Machine in Verilog

```

case (state)
  ST_IDLE:
    if (num[5])
      next_state = ST_5;
  ST_5: begin
    if (num[4])
      next_state = ST_4;
    else if (num[5])
      next_state = ST_5;
    else if ( (|num) | e ) //other btns
      next_state = ST_IDLE;
  end
  ST_4: begin
    if (num[3])
      next_state = ST_UL;

```

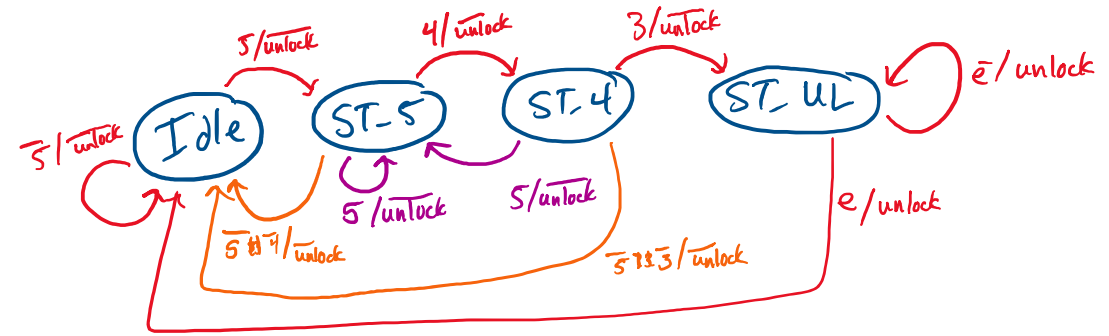


```

    else if (num[5])
      next_state = ST_5;
    else if ( (|num) | e ) // other btns
      next_state = ST_IDLE;
  end
  ST_UL: begin
    unlock = 1'h1;
    if (e)
      next_state = ST_IDLE;
  end
endcase



```


Glitch

 

Flip-Flop Timing

- Assume 5ps/ Gate

 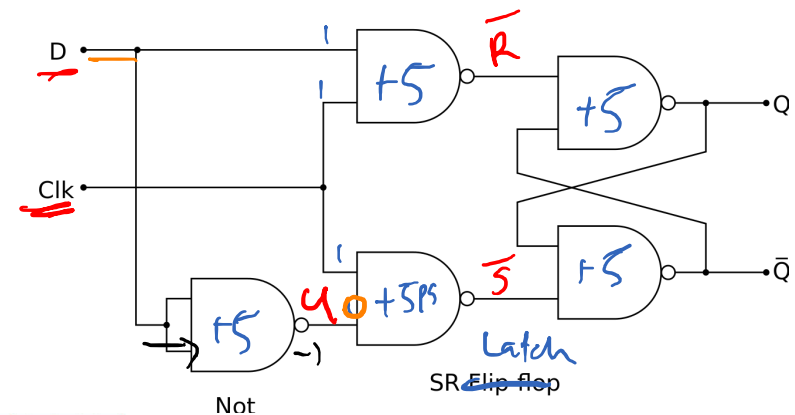


FIXME

Setup and Hold Time

- **Setup Time:** minimum time the inputs to a flip-flop must be stable before the clock edge
- **Hold Time:** minimum time the inputs to a flip-flop must be stable after the clock edge

Setup/Hold Time

Setup/Hold Time

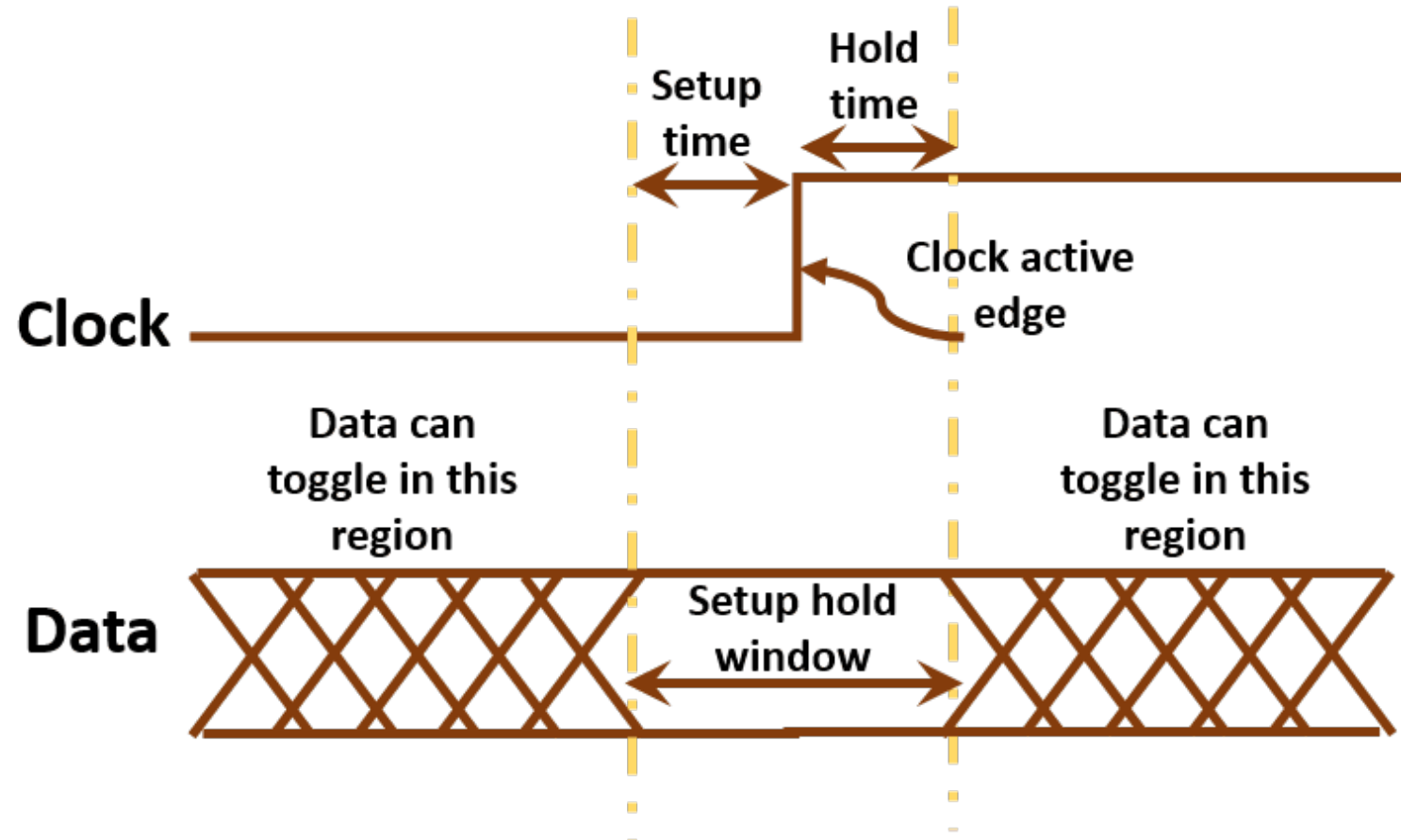


Intra Flip-Flop Timing

Inter Flip-Flop Timing

Intra Flip-Flop Timing

Register to register timing:

 - output of a register $Q1$
- some combinational circuit
- input to the next register $D2$




Delays:

- t_{co} , clock to output delay,
- t_{pd} , propagation delay in combinational circuit
- t_c , clock period

Timing requirement:


$$t_{co} + t_{pd} + t_{su} < t_c$$

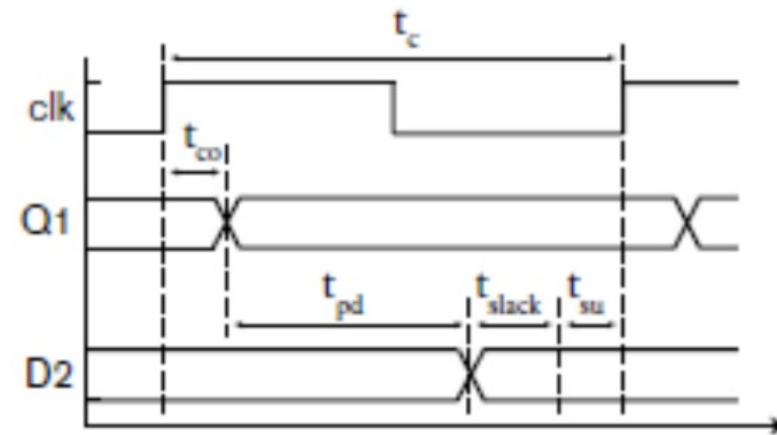

Slack

- Extra time between combinational propagation delay and setup time
- Time between stable input to Flip-Flop and next clock edge

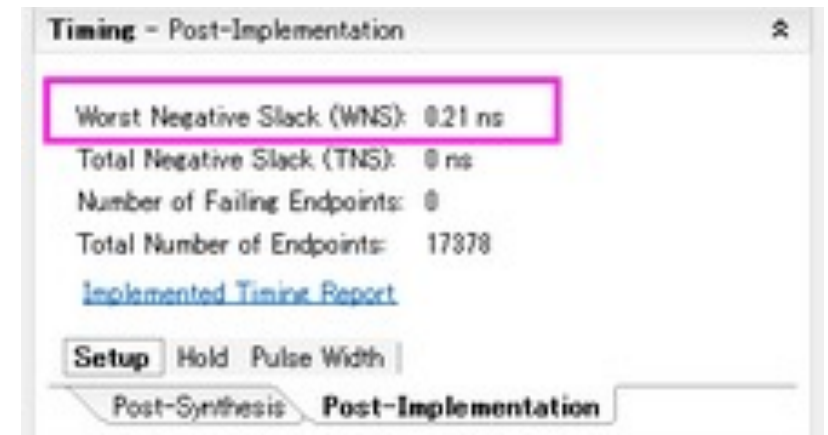- Vivado:
 - WNS: Worst-case Negative Slack



- If this number is <0 , your circuit will (probably) not work

`for (; ;)` Loops in Verilog

- Testbenches – just like C/C++
- Synthesizable modules - more like `#define`

`for (; ;)` Loops in Verilog

- Testbenches – just like C/C++
- Synthesizable modules - more like `#define`
- `for (; ;)` loop is expanded at **Compile (Synthesis) Time**

Correct for (; ;) Loops in Verilog


```
module MysteryFunction(  
    input[3:0] a,  
    input[1:0] right,  
    output[3:0] y  
);  
  
    //correct for loop  
    integer x; // OR genvar x  
    for (x = 0; x < 4; x++) begin  
        assign y[x] = a[x+right];  
    end  
  
endmodule
```

Correct for (; ;) Loops in Verilog

```
module RightBarrelShift (  
    input[3:0] a,  
    input[1:0] right,  
    output[3:0] y  
);
```

```
//correct for loop  
integer x; // OR genvar x  
for (x = 0; x=0 x < 4; x++) begin  
    assign y[x] = a[x+right];  
end
```

```
endmodule
```

 

assign y[0] = a[0+right]
assign y[1] = a[1+right]
...

Correct for (; ;) Loops in Verilog

This Code:

```
integer x; //or genvar x
for (x = 0; x < 4; x++) begin
    assign y[x] = a[x+right];
end
```

Expands to:

```
assign y[0] = a[0 + right];
assign y[1] = a[1 + right];
assign y[2] = a[2 + right];
assign y[3] = a[3 + right];
```

Incorrect `for (; ;)` Loops in Verilog

```
integer i;
wire carry;

for(i = 0; i < 4; i++) begin
    if (i == 0) begin
        assign sum[i] = a[i] ^ b[i] ^ c_in;
        assign carry = a[i] & b[i] | a[i] & c_in | b[i] & c_in;
    end else begin
        assign sum[i] = a[i] ^ b[i] ^ carry;
        assign carry = a[i] & b[i] | a[i] & carry | b[i] & carry;
    end
end

end
assign c_out = carry;
```

What is wrong here?

Incorrect `for (; ;)` Loops in Verilog

```
integer i;
wire carry;

for(i = 0; i < 4; i++) begin
    if (i == 0) begin
        assign sum[i] = a[i] ^ b[i] ^ c_in;
        assign carry = a[i] & b[i] | a[i] & c_in | b[i] & c_in;
    end else begin
        assign sum[i] = a[i] ^ b[i] ^ carry;
        assign carry = a[i] & b[i] | a[i] & carry | b[i] & carry;
    end
end

end
assign c_out = carry;
```

What is wrong here?

Incorrect `for (; ;)` Loops in Verilog

```
integer i;
wire carry;
assign sum[0] = a[0] ^ b[0] ^ c_in;
assign carry = a[0] & b[0] | a[0] & c_in | b[0] & c_in;
assign sum[1] = a[1] ^ b[1] ^ carry;
assign carry = a[1] & b[1] | a[1] & carry | b[1] & carry;
assign sum[2] = a[2] ^ b[2] ^ carry;
assign carry = a[2] & b[2] | a[2] & carry | b[2] & carry;
assign sum[3] = a[3] ^ b[3] ^ carry;
assign carry = a[3] & b[3] | a[3] & carry | b[3] & carry;
assign c_out = carry;
```

Correcting `for (; ;)` Loops in Verilog

```
integer i;
wire carry;

for(i = 0; i < 4; i++) begin
    if (i == 0) begin
        assign sum[i] = a[i] ^ b[i] ^ c_in;
        assign carry = a[i] & b[i] | a[i] & c_in | b[i] & c_in;
    end else begin
        assign sum[i] = a[i] ^ b[i] ^ carry;
        assign carry = a[i] & b[i] | a[i] & carry | b[i] & carry;
    end
end

end
assign c_out = carry;
```

How do we fix this?

Correcting `for (; ;)` Loops in Verilog

```
integer i;
wire [3:0] carry;

for(i = 0; i < 4; i++) begin
    if (i == 0) begin
        assign sum[i] = a[i] ^ b[i] ^ c_in;
        assign carry[i] = a[i] & b[i] | a[i] & c_in | b[i] & c_in;
    end else begin
        assign sum[i] = a[i] ^ b[i] ^ carry[i-1];
        assign carry[i] = a[i] & b[i] | a[i] & carry[i-1] | b[i] & carry[i-1];
    end
end

end
assign c_out = carry[3];
```


How do we fix this?

Correcting for (; ;) Loops in Verilog

```
integer i;
wire carry;
assign sum[0] = a[0] ^ b[0] ^ c_in;
assign carry[0] = a[0] & b[0] | a[0] & c_in | b[0] & c_in;
assign sum[1] = a[1] ^ b[1] ^ carry[0];
assign carry[1] = a[1] & b[1] | a[1] & carry[0] | b[1] & carry[0];
assign sum[2] = a[2] ^ b[2] ^ carry[1];
assign carry[2] = a[2] & b[2] | a[2] & carry[1] | b[2] & carry[1];
assign sum[3] = a[3] ^ b[3] ^ carry[2];
assign carry[3] = a[3] & b[3] | a[3] & carry[2] | b[3] & carry[2];
assign c_out = carry[3];
```

Serial Communication



- Do you remember this circuit?

 


- What did it do?

Converts serial input to parallel output


Shift Register

  

What does this circuit do?

 


What about this circuit?

 


Serial Peripheral Interface (SPI)


- The **Serial Peripheral Interface (SPI)** is a synchronous **serial communication interface** specification used for short-distance communication, primarily in embedded systems.
- SPI devices **communicate in full duplex** mode using a master-slave architecture. The master (controller) device **originates the frame for reading and writing**. Multiple slave-devices may be supported through selection with individual chip select (CS), sometimes called slave select (SS) lines.
- [Wiki]

SPI

 


 



When to CAPTURE new data?

 

When to SEND new data?

 

SPI Example

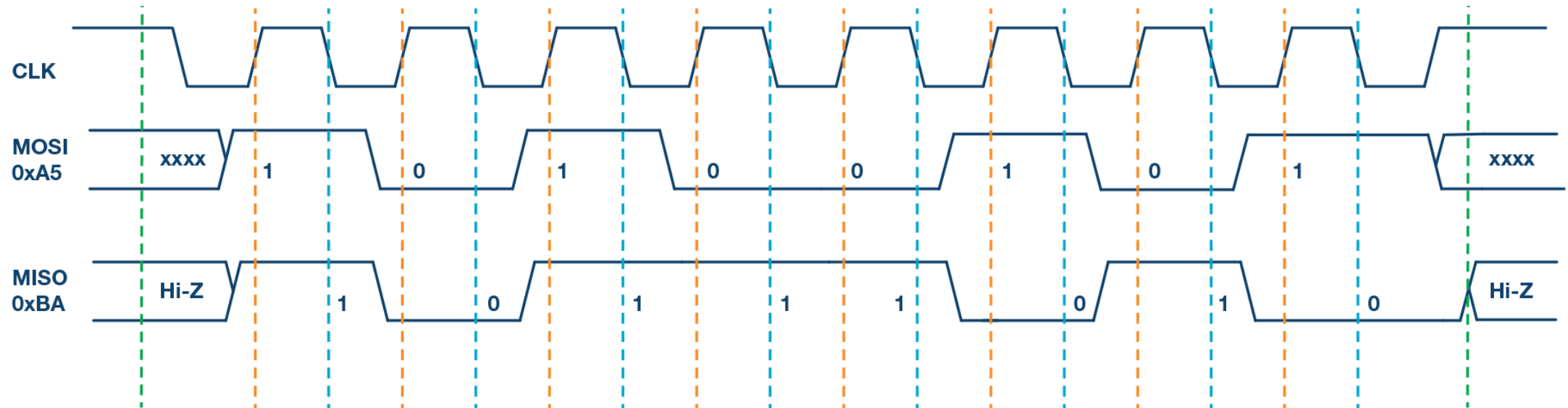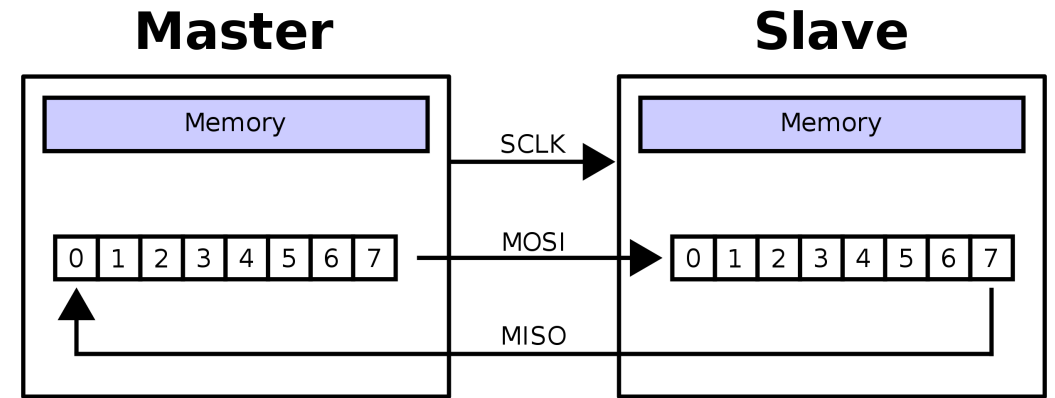

Next Time

- clk vs CLOCK
- Synchronizers