

ENGR 210 / CSCI B441  
“Digital Design”

# Memory

Andrew Lukefahr

# Announcements

- P9 – SPI
  - This one is new. Might be some changes.
  - Last one
- Final: ~~Thursday~~ 5/6 @ 12.40-2:40pm

Friday

Fixme!

# P9 SPI QuickStart

- We build the Vivado project for you:

```
git clone https://github.com/ENGR210/P9\_SPI.git  
cd P9_SPI  
make setup  
vivado vivado/vivado.xpr
```

- We provide you with Testbenches
- Same ones as the Autograder!


# ROM vs RAM

- ROM – Read-Only Memory
  - Input: address
  - Output: fixed value
- RAM – Random-Access Memory
  - Read/Write version of a ROM


# Rom Cell

# Array of ROM Cells

# 2-bit ROM

 

## 2-bit ROM of AND + OR

 



# ROM in Verilog

```
module ROM (  
    input [1:0] addr,  
    output [3:0] data  
)  
    logic [3:0] array [0:3]; //2D Array  
    assign array = { 4'b0011, 4'b0110, 4'b0101, 4'b1100}  
    assign data = array[addr];  
endmodule
```


# RAM

- Similar to ROM
- BUT WRITABLE!

# RAM


- Similar to ROM
- BUT WRITABLE!

Rom Cell

 

# 4-bit RAM

# Array of 4-bit RAM

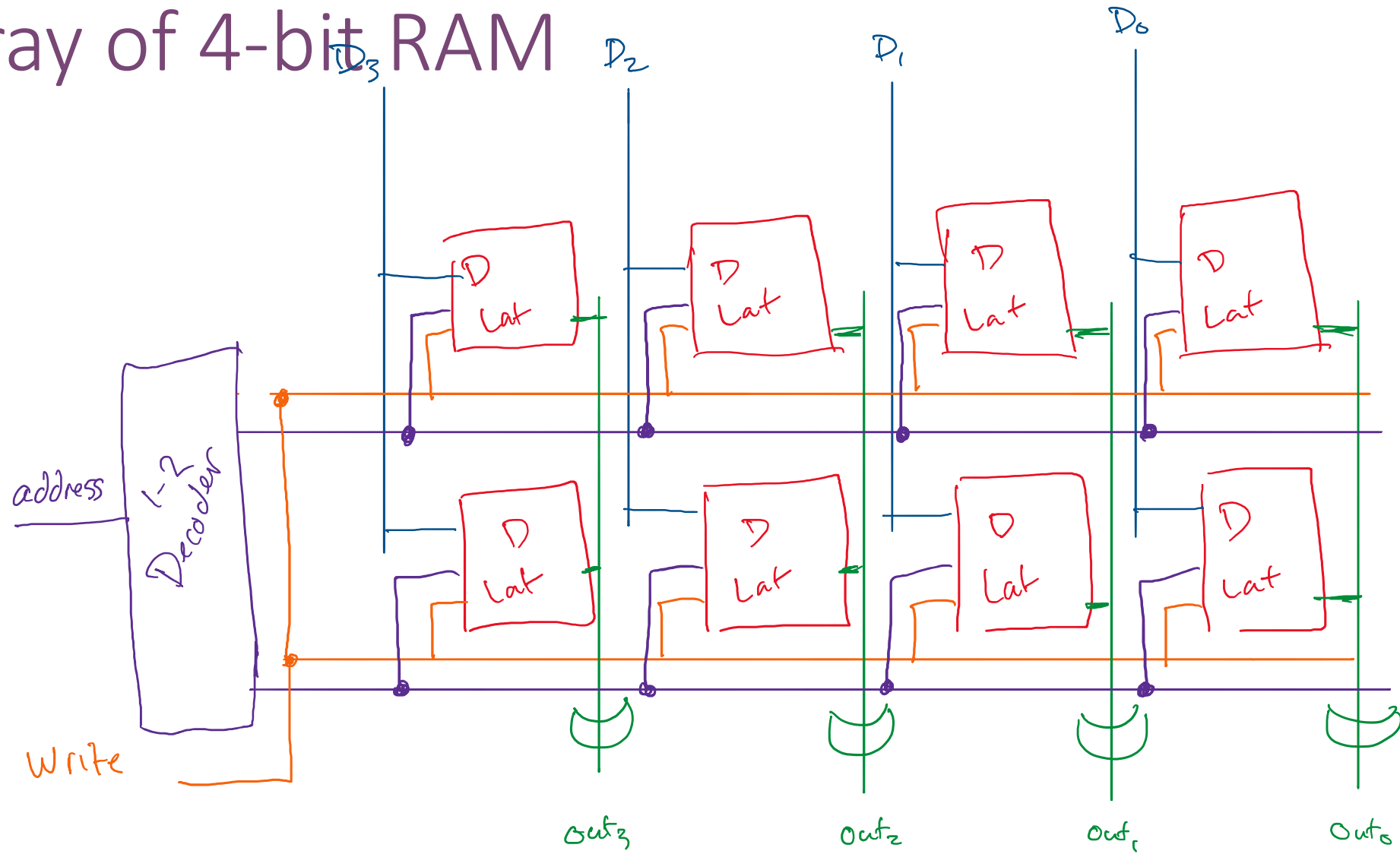

# Flip-Flop RAM in Verilog

```
module RAM (  
    input      clk,  
    input [1:0] addr,  
    input      set,  
    input [3:0] set_data,  
    output [3:0] read_data  
)  
    logic [3:0] array [0:3]; //2D Array  
  
    assign read_data = array[addr];  
endmodule
```

# Flip-Flop RAM in Verilog

```
module RAM (  
    input      clk,  
    input [1:0] addr,  
    input      set,  
    input [3:0] set_data,  
    output [3:0] read_data  
)  
    logic [3:0] array [0:3]; //2D Array  
    always_ff @(posedge clk) begin  
        if (set) array[addr] <= set_data;  
    end  
    assign read_data = array[addr];  
endmodule
```

# Aside: Latch RAM in Verilog

```
module RAM (
```

← does not need clk

```
    input [1:0] addr,
```

```
    input      set,
```

```
    input [3:0] set_data,
```

```
    output [3:0] read_data
```

```
)
```

```
    logic [3:0] array [0:3]; //2D Array
```

→ **always\_latch begin** //if you really want a latch

```
        if (set) array[addr] = set_data; ← not have default
```

```
    end
```

```
    assign read_data = array[addr];
```

```
endmodule
```

Any glitch on set will kill this.  
Do not use in class!



# Can I make this into an AND gate?

```
module RAM (  
    input      clk,  
    input [1:0] addr,  
    input      set,  
    input [3:0] set_data,  
    output [3:0] read_data  
)  
    logic [3:0] array [0:3]; //2D Array  
    always_ff @(posedge clk) begin  
        if (set) array[addr] <= set_data;  
    end  
    assign read_data = array[addr];  
endmodule
```

# Look-Up Table (LUT)


- DON'T compute a Boolean equation
- DO pre-compute all solutions in a table
- DO look up the Boolean result in the table

- Examples:

$s = a \wedge b;$

$c = a \& b;$

# Full-Adder LUT

 

Input			Output	
A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# LUT size

- Why not a 1000-input,100-output LUT?
- 3 inputs  $\Rightarrow 2^3$  rows = 8 rows
- 4 inputs  $\Rightarrow 2^4$  rows = 16 rows
- 5 inputs  $\Rightarrow 2^5$  rows = 32 rows
- ...
- 64 inputs  $\Rightarrow 2^{64}$  rows =  $1.85 \times 10^{19}$  rows
- LUT input size does not scale well.

# Divide and Conquer with LUTs

- 3-Bit Full Adder

# Sequential Logic

- Problem: How do we handle sequential logic?
  - LUTs cannot contain state
- Solution: Add a Flip-Flop

# Basic Logic Element

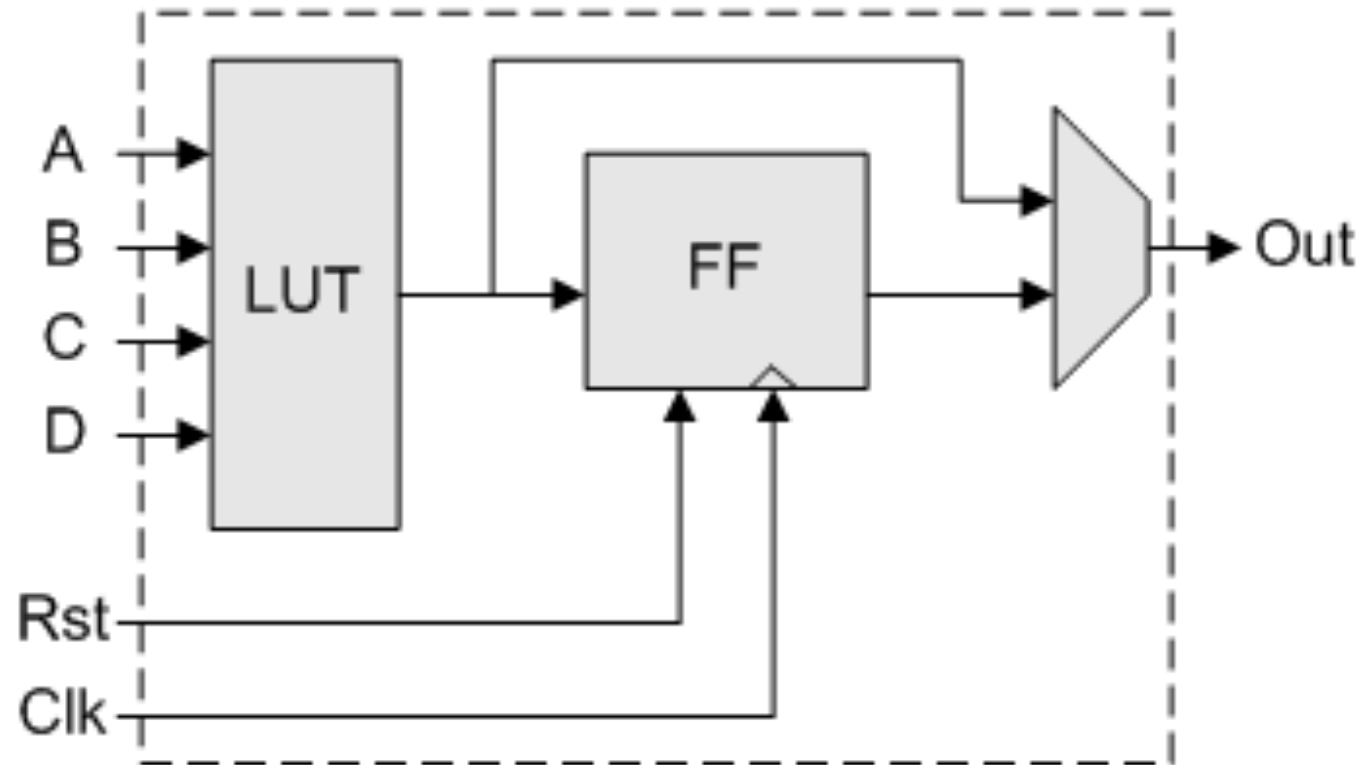


Fig.4 Example of Configurable Logic Cell.

# Basic Logic Element

- What if I only want to store a value?


 



Fig.4 Example of Configurable Logic Cell.

 

# Configurable Logic Block (CLB)








# Configurable Logic Block (CLB)

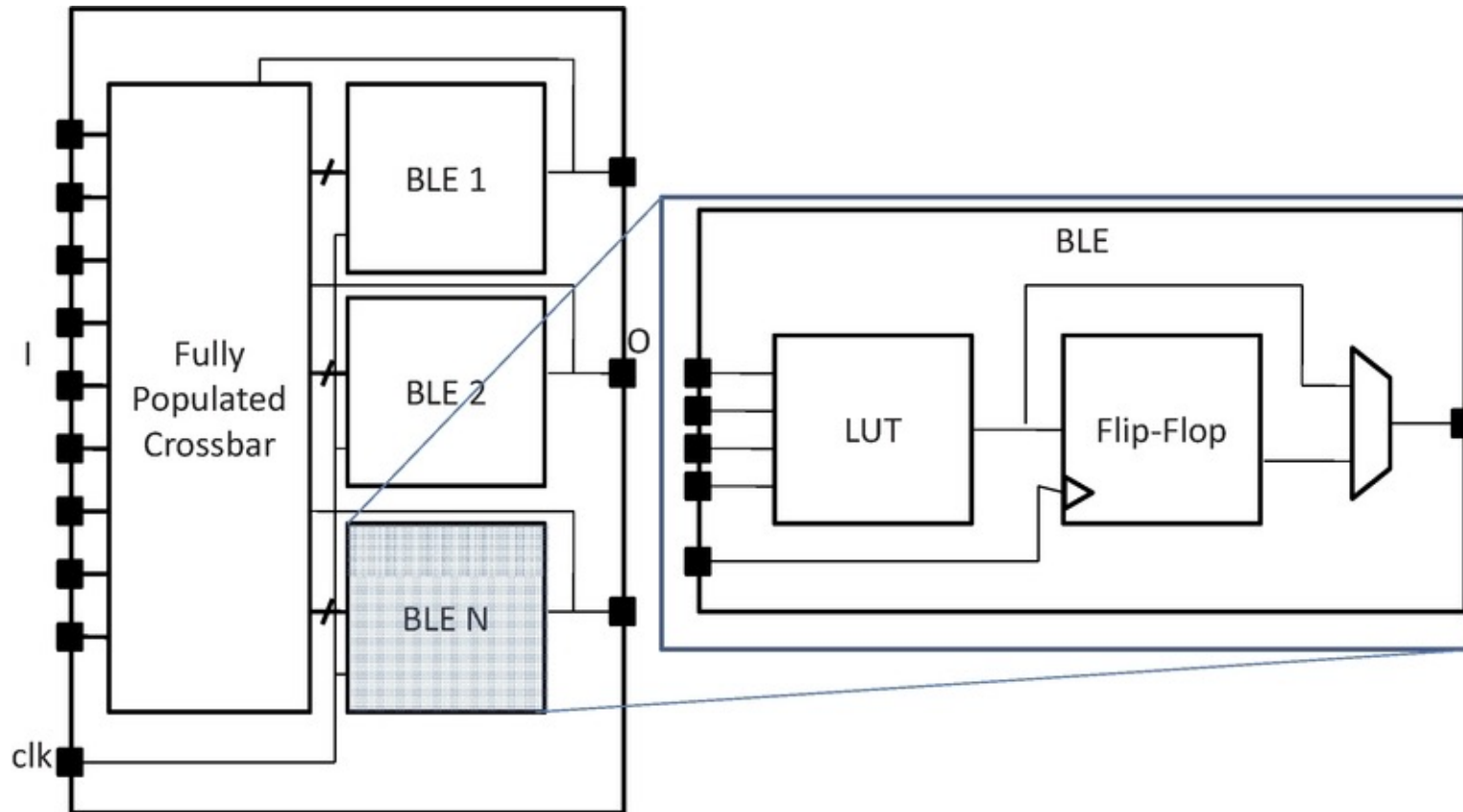

     
# Connecting CLBs

- Q: How do CLBs talk to each other?
- A: Put wires everywhere!



 
# Connecting CLBs

- Q: How do CLBs talk to each other?
- A: Put wires everywhere (ok, almost everywhere)!



 
# How to connect CLBs to wires?

- “Connection box”
  - Device that allows inputs and outputs of CLB to connect to different wires




# Connection Box Flexibility

 

*\*Dots represent **possible** connections*

 
# Switch Box

- Connects horizontal and vertical routing channels



 
# Switch Box Connections

- Programmable connections between inputs and outputs





*Wilton*

 


*\*Not all possible  
connections shown*



# Switch Box Connections

  


# How to connect wires to each other?

 

# FPGA “Fabric”


- 2D array of CLBs + interconnects

 

- Am I missing anything?


# Block RAM

- Special blocks of just RAM

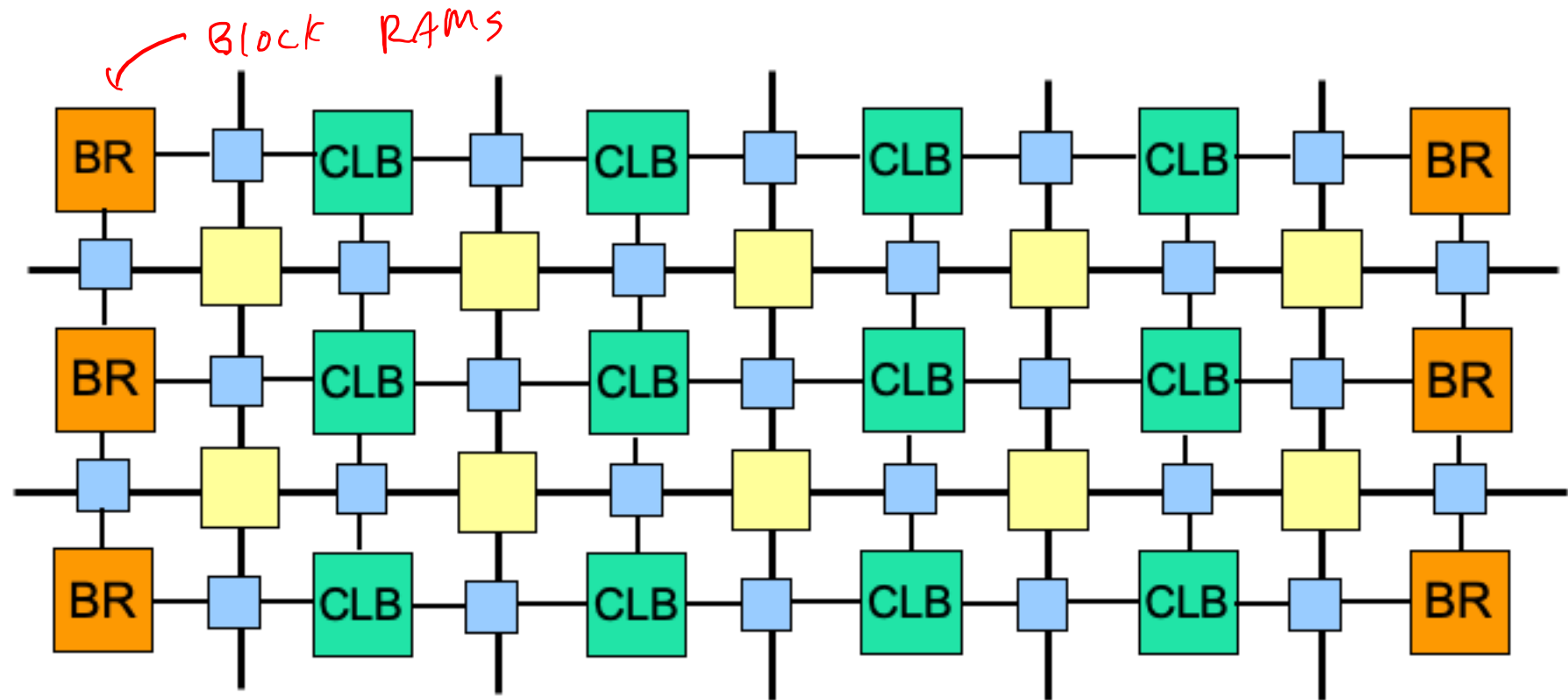


DSPs → Digital Signal Processor → dedicated math units

multiply

 

# Input/Output (IO)

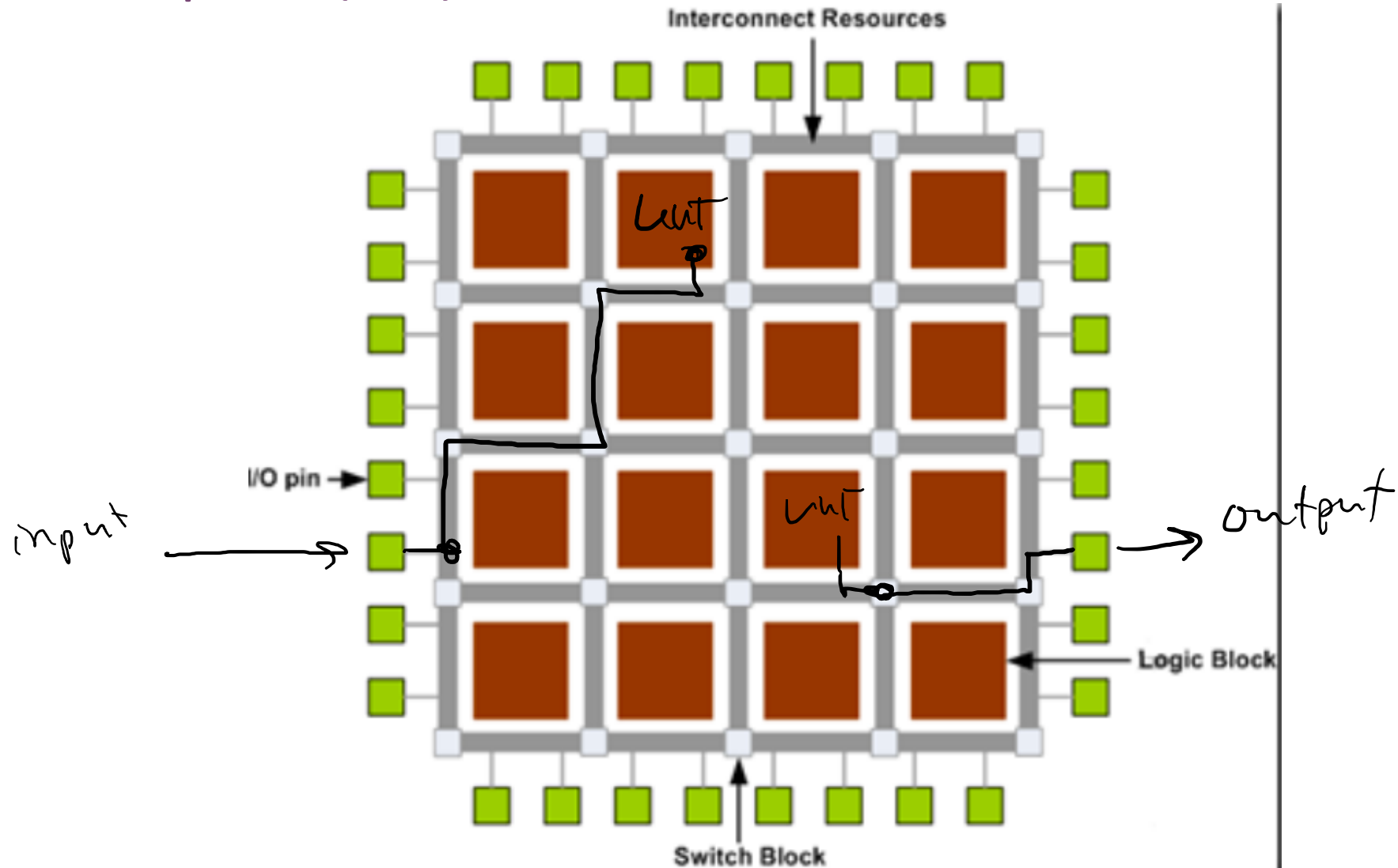

# Next Time

- What's next?
- Review