

ENGR 210 / CSCI B441
“Digital Design”

Final Review

Andrew Lukefahr

Announcements

- P5 due next Friday!
- Exam on Tuesday (!?!?)
- Notice: 2 major deadlines, 1 week!
 - Start EARLY!!!!

General Topics

- Truth Tables / Boolean Logic / Logic Gates
- Combinational Logic
- ALU
- RS, D Latch, D Flip Flop Circuits
- State Machines
- SPI
- FPGAs

Textbook Mapping

Chapter Section

- Section 1.2

- Section 2.2 (skip 2.2.2)

- Section 2.3

- Section 2.4

- Section 3.1

- Section 3.2

- Section 4.1

- Section 4.2

- Section 4.3

{ unsigned & signed
arith

{ comb

{ seq logic

Verilog on Exam (?)

- Oh, yes!
- Big part of the exam is writing Verilog.
- Don't care about minor syntax errors
 - Missing commas / semi-colons (;)
- Minor point deductions for:
 - Blocking vs. Non-blocking operators
 - Missing delays (#)
- Major point deductions for logical errors!

=


<=

A “Cheat” Sheet is Allowed


- 1-sided
 - 8.5”x11” paper
 - Handwritten (not photocopied)
-
- Keep this, you can use the other side for the 2nd exam.

Logic Gates


Logic Gates

 

X NOR

 


XOR

 

NAND



NOR

 

Boolean Equation -> Truth Table

Write the truth table for the following Boolean equation:

$$y = (ab + ca) \oplus bc$$

$$y = ((a \& b) \mid (c \& d)) \wedge (b \& c);$$

Boolean Equation -> Truth Table

Write the truth table for the following Boolean equation:

$$y = (ab + ca) \oplus bc$$

<u>a</u>	<u>b</u>	<u>c</u>	<u>y</u>	<u>ab</u>	<u>ca</u>	<u>ab+ca</u>	<u>bc</u>	<u>y = (ab+ca) ⊕ bc</u>
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	1	1
0	1	1	1	0	0	0	1	0
1	0	0	1	0	0	0	0	1
1	0	1	1	0	1	1	0	1
1	1	0	1	1	0	1	0	1
1	1	1	0	1	1	1	1	0

Truth Table -> Boolean Equation

A	B	C	D	X	Y
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	1	0
0	1	0	0	0	1
0	1	0	1	0	0
0	1	1	0	0	0
0	1	1	1	1	0
1	0	0	0	0	0
1	0	0	1	0	1
1	0	1	0	0	0
1	0	1	1	1	0
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	1
1	1	1	1	1	0

Truth Table -> Boolean Equation

**not need to be minimized*

A	B	C	D	X	Y
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	1 ^{x1}	0
0	1	0	0	0	1
0	1	0	1	0	0
0	1	1	0	0	0
0	1	1	1	1 ^{x2}	0
1	0	0	0	0	0
1	0	0	1	0	1
1	0	1	0	0	0
1	0	1	1	1 ^{x3}	0
1	1	0	0	1 ^{x4}	0
1	1	0	1	1 ^{x5}	0
1	1	1	0	1 ^{x6}	1
1	1	1	1	1 ^{x7}	0

$$X = x_1 \mid x_2 \mid x_3 \mid x_4 \mid x_5 \mid x_6 \mid x_7$$

$$x = \bar{a}\bar{b}cd \mid \bar{a}bcd \mid a\bar{b}cd \mid$$




$$abc\bar{d} \mid ab\bar{c}d \mid abc\bar{d} \mid abcd$$

$$y = \bar{a}b\bar{c}\bar{d} \mid a\bar{b}\bar{c}d \mid$$

$$abcd$$

$$y = \bar{A} B \bar{C} \bar{D} + A \bar{B} \bar{C} D + A B C \bar{D}$$
   
$$y = \bar{A} B \bar{C} \bar{D} + A \bar{B} \bar{C} D + A B C \bar{D}$$



Multiplexer in Verilog

```
module mux (  
    input [7:0] raw,  
    input [2:0] select,  
    output out  
);
```

```
endmodule
```

Multiplexer in Verilog

```
module mux (
    input [7:0] raw,
    input [2:0] select,
    output out
    or "output reg out"
);
```

```
    reg outR;
    always_comb begin
```

```
        case (select)
```

```
            3'h0: outR = raw[0];
```

```
            3'h1: outR = raw[1];
```


```
            3'h2: outR = raw[2];
```

```
            3'h3: " " [3]
```

```
        endcase
```

```
    endmodule
```

```
    assign out = outR;
```

 

```
... raw[4]
    {5}
    {6}
    {7}
```


Multiplexer in Verilog

```
module mux (  
    input [7:0] raw,  
    input [2:0] select,  
    output logic out  
);  
  
always_comb begin  
    case (select)  
        3'h0: out = raw[0];  
        3'h1: out = raw[1];  
        3'h2: out = raw[2];  
        3'h3: out = raw[3];  
        3'h4: out = raw[4];  
        3'h5: out = raw[5];  
        3'h6: out = raw[6];  
        3'h7: out = raw[7];  
    endcase  
end  
endmodule
```

Multiplexer in Verilog

```
module mux (  
    input [7:0] raw,  
    input [2:0] select,  
    output out  
);  
  
    assign out = raw[ select ]; // :)  
  
endmodule
```

MUX Testbench

```
module mux (  
    input [7:0] raw,  
    input [2:0] select,  
    output out  
);
```

MUX Testbench

```
module testbench;
  logic [7:0] raw;
  logic [2:0] sel;
  logic out



  mux m0 (.raw(raw), .select(sel), .out(out));

  integer i, j;
  initial begin
    for (i = 0; i < 256; i++) begin
      for (j = 0; j < 8; j++) begin
        raw = i; sel = j;
        #1
        assert(out == raw[sel]) else $fatal(1, "Bad Out");
      end
    end
  end
end


endmodule
```

<- Could also use Task here!

Timing Diagram

  

Example: Traffic Signal Controller

 

The main highway gets priority, should be normally green.


Cars from a country cause the traffic signal to turn green only long enough to let the cars on the country road go.

There is a sensor to detect cars waiting on the country road. The sensor sends a signal X as input to the controller:

$X = 1$, if there are cars on the country road


$X = 0$, otherwise

What are the `States`?

 


What are the 'States'?

Moore Type

 


What are the 'States'?

 

State Machine

Mealy Type

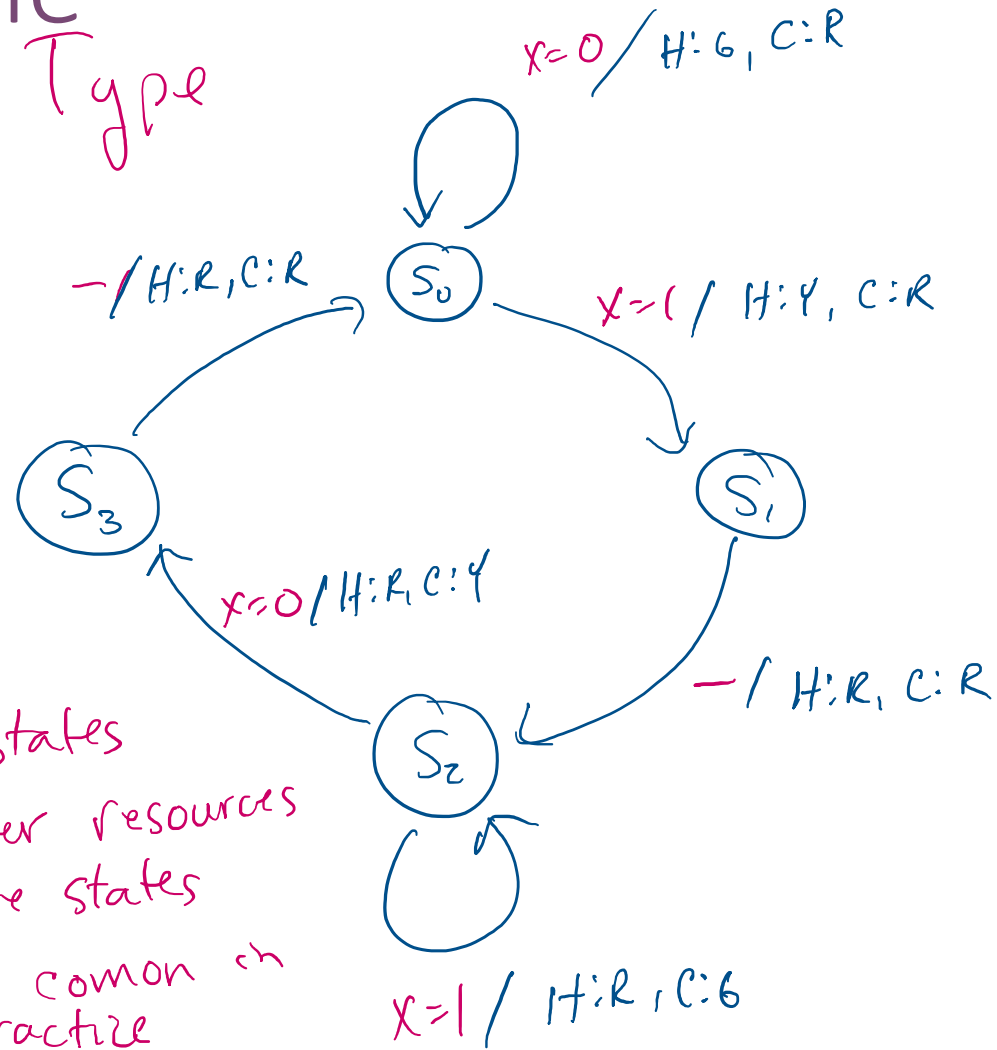

Mealy Type:

- needs less states
- needs fewer resources to store states
- is more common in practice

What's the FSM here?


```
module ReverseEngr (  
    input clk, rst,  
    input X,  
    output Y,  
);  
  
enum {S0, S1} state, nextstate;  
  
always_ff (@posedge clk) begin  
    if (rst) state <= S0;  
    else  
        state <= nextstate;  
end
```

```
always_comb begin  
    Y = 1'b0;  
    case (state)  
        S0: begin  
            if (x) begin  
                Y = 1;  
                nextstate = S1  
            end else begin  
                nextstate = S0;  
            end  
  
        S1: begin  
            if (X)  
                nextstate = S0;  
            else begin  
                Y = 1;  
                nextstate = S1;  
            end  
        end  
    endcase  
end  
endmodule
```

What's the FSM here?


```
module ReverseEngr (  
    input clk, rst,  
    input X,  
    output Y,  
);  
  
enum {S0, S1} state, nextstate;  
  
always_ff (@posedge clk) begin  
    if (rst) state <= S0;  
    else  
        state <= nextstate;  
end
```

What's the FSM here?

 


```
always_comb begin
    Y = 1'b0;
    case (state)
        S0: begin
            if (x) begin
                Y = 1;
                nextstate = S1
            end else begin
                nextstate = S0;
            end

         S1: begin
            if (X)
                nextstate = S0;
            else begin
                Y = 1;
                nextstate = S1;
            end
        end
    endcase
end
endmodule
```




SPI

- Incoming Data:

 

- Outgoing Data:

Finding SCLK Edges

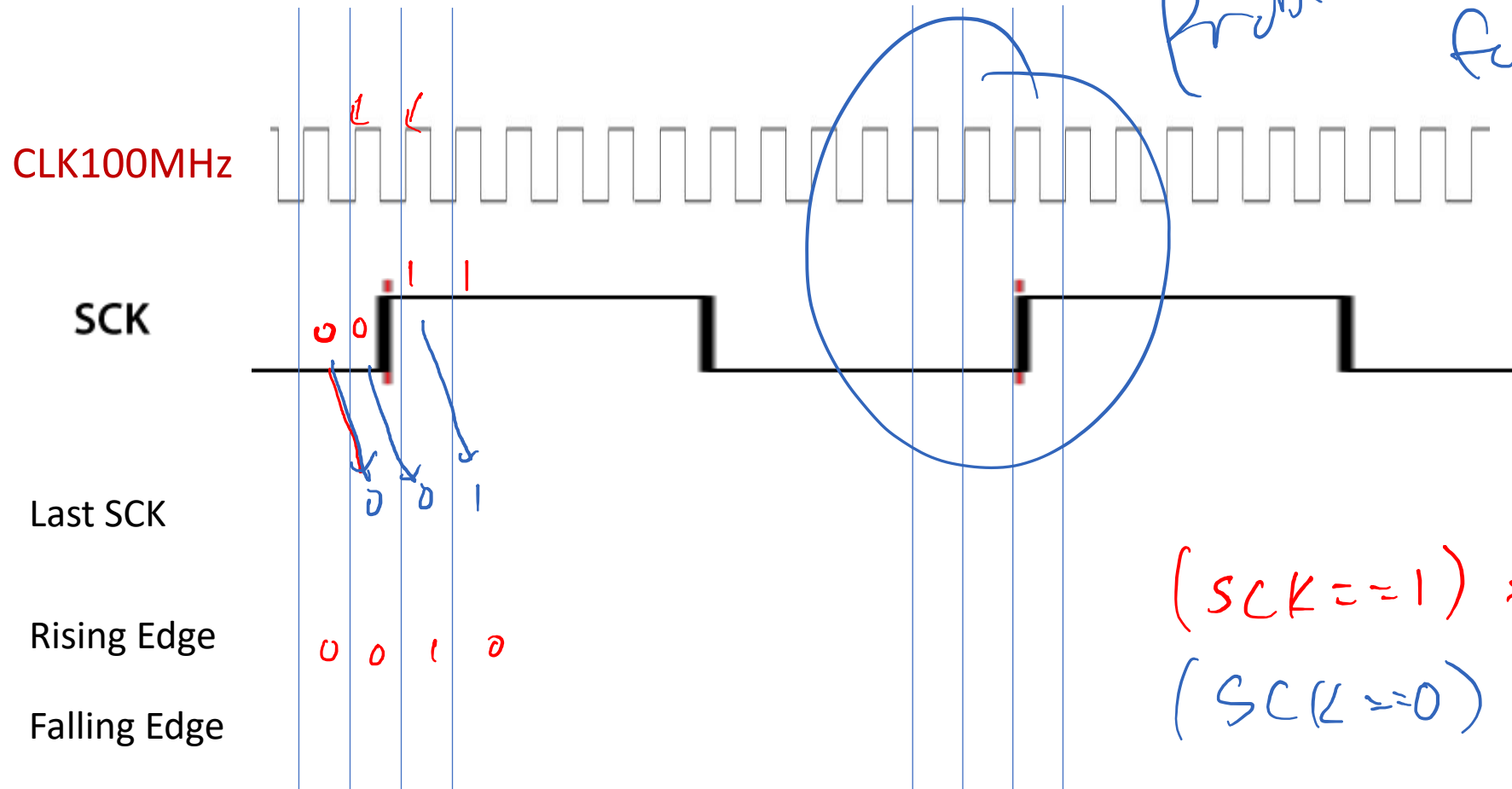


Write Protocol

Operation: WRITE ('h0)

Address: LEDs ('h3)

Data: ON-OFF-ON-OFF ('b10101010)

 


Read Protocol

Operation: READ (`h1)

Address: SWITCHES (`h1)

Data: ??

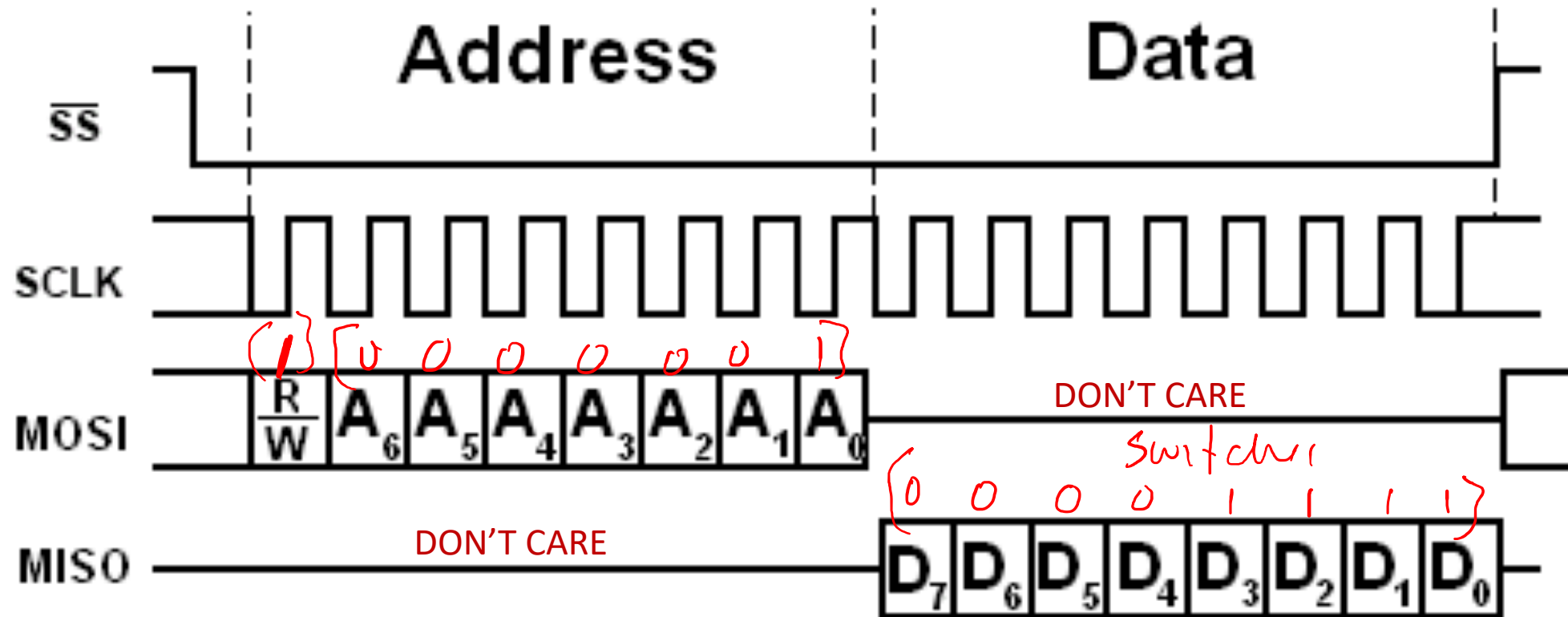

[pyroelectro]