

ENGR 210 / CSCI B441

Testbenches/ Addition / Subtraction

Andrew Lukefahr

Announcements

- P5 is due Friday
- P6 is out

A simple testbench

```
`timescale 1ns/1ps
module BeltAlarm_tb();

    logic k, p, s;
    logic alarm; //or 'wire'
    BeltAlarm dut0( .k(k), .p(p), .s(s), .alarm(alarm) );

    initial
    begin
        k = 'h0; p = 'h0; s= 'h0;
        $monitor ("k:%b p:%b s:%b a:%b", k, p, s, alarm);
        #10
        assert(alarm == 'h0) else $fatal(1, "bad alarm");
        $display("@@@Passed");
    end
endmodule
```

```
module BeltAlarm(
    input k, p, s,
    output alarm
);

    assign alarm = k & p & ~s;
endmodule
```

BeltAlarm Testing

```
initial
begin
    k = 'h0; p = 'h0; s = 'h0;
    $monitor ("k:%b p:%b s:%b a:%b",
              k, p, s, alarm);
    checkAlarm('h0,'h0,'h0,'h0);
    checkAlarm('h0,'h0,'h1,'h0);
    checkAlarm('h0,'h1,'h0,'h0);
    checkAlarm('h0,'h1,'h1,'h0);
    checkAlarm('h1,'h0,'h0,'h0);
    checkAlarm('h1,'h0,'h1,'h0);
    checkAlarm('h1,'h1,'h0,'h1);
    checkAlarm('h1,'h1,'h1,'h0);
    $display("@@@Passed");
end
```

```
task checkAlarm(
    input kV, stPasV, sbPasV,
    input stDrvV, sbDrvV,
    input alarmV
);

    k = kV; stPas=stPasV, sbPas=sbPasV;
    stDrv = stDrvV; sbDrv = sbDrvV;
    #10
    assert(alarm == alarmV) else
        $fatal (1, "bad alarm, expected:%b got:%b",
                alarmV, alarm);
endtask
```

Submodule Example

```
`timescale 1 ns/1 ns

module TwoBeltAlarm(
    input k, st_pas, sb_pas,
    input st_drv, sb_drv
    output alarm
);

    logic al_pas, al_drv; //or `wires`

    //submodules, two different examples
    BeltAlarm ba_drv(k, st_drv, sb_drv, al_drv); //no named arguments
    BeltAlarm ba_pas(.k(k), .p(st_pas),
        .s(sb_pas), .alarm(al_pas)); // with named arguments

    assign alarm = al_pas | al_drv;
endmodule
```

```
`timescale 1 ns/1 ns

module BeltAlarm(
    input k, p, s,
    output alarm
);

    assign alarm = k & p & ~s;

endmodule
```

2-BeltAlarm testbench

```
`timescale 1ns/1ps
module tb();

  logic k, p, s;
  logic alarm;

  BeltAlarm dut0( .k(k), .p(p), .s(s), .alarm(alarm) );

  initial
  begin
    k = 'h0; p = 'h0; s = 'h0;
    $monitor ("k:%b p:%b s:%b a:%b", k, p, s, alarm);
    #10
    assert(alarm == 'h0) else $fatal(1, "bad alarm");
    $display("@@@Passed");
  end
endmodule
```

```
module TwoBeltAlarm(
  input k, st_pas, sb_pas,
  input st_drv, sb_drv,
  output alarm
);
  logic al_pas, al_drv;

  BeltAlarm ba_drv(k, st_drv, sb_drv, al_drv);
  BeltAlarm ba_pas(.k(k), .p(st_pas),
    .s(sb_pas), .alarm(al_pas));

  assign alarm = al_pas | al_drv;
endmodule
```

2-BeltAlarm Task

```
task checkAlarm(  
    input kV, stPasV, sbPasV,  
    input stDrvV, sbDrvV,  
    input alarmV  
);  
  
    k = kV; stPas=stPasV, sbPas=sbPasV;  
    stDrv = stDrvV; sbDrv = sbDrvV;  
    #10  
    assert(alarm == alarmV) else  
        $fatal (1, "bad alarm, expected:%b got:%b",  
                alarmV, alarm);  
  
endtask
```

```
module TwoBeltAlarm(  
    input k, st_pas, sb_pas,  
    input st_drv, sb_drv  
    output alarm  
);  
    logic al_pas, al_drv;  
  
    BeltAlarm ba_drv(k, st_drv, sb_drv, al_drv);  
    BeltAlarm ba_pas(.k(k), .p(st_pas),  
                    .s(sb_pas), .alarm(al_pas));  
  
    assign alarm = al_pas | al_drv;  
endmodule
```

```

initial begin
    k = 0; st_pas = 'b0; sb_pas = 'b0;
    st_drv = 'b0; sb_drv = 'h0;
    #10
    assert(alarm == 'h0) else $fatal(1, "bad alarm");
    #10
    checkAlarm(0,'b0,'h0, 'h0, 'h0, 'h0);
    for (int i = 0; i < 32; ++i) begin
        $display("i:%d [%b]", i, i[4:0]);

        if ( (i == 18) | (i == 22) | (i == 30)) // driver
            checkAlarm( i[4], i[3], i[2], i[1], i[0], 'h1);
        else if ( (i == 24 ) | (i == 25) | (i==27)) //passenger
            checkAlarm( i[4], i[3], i[2], i[1], i[0], 'h1);
        else if ( (i==26) ) //both
            checkAlarm( i[4], i[3], i[2], i[1], i[0], 'h1);
        else
            checkAlarm( i[4], i[3], i[2], i[1], i[0], 'h0);
    end

    $display("@@@Passed");

end

```

```

task checkAlarm(
    input kV, stPasV, sbPasV,
    input stDrvV, sbDrvV,
    input alarmV
);

    k = kV; stPas=stPasV, sbPas=sbPasV;
    stDrv = stDrvV; sbDrv = sbDrvV;
    #10
    assert(alarm == alarmV) else
        $fatal (1, "bad alarm, expected:%b got:%b",
            alarmV, alarm);

endtask

```


For Loops in Testbenches

- You can write for-loops in your testbenches

```
module for_loop_simulation ();  
    logic [7:0] r_Data; // Create 8 bit value  
  
    initial begin  
        for (int ii=0; ii<6; ii=ii+1) begin  
            r_Data = ii;  
            $display("Time %d: r_Data is %b", $time, r_Data);  
            #10;  
        end  
    end  
endmodule
```

- Please **no for-loops in your synthesizable code (yet)!**

```

`timescale 1ns/1ps
module tb();

logic k, st_pas, sb_pas, st_drv, sb_drv;
logic alarm;

TwoBeltAlarm dut0(
    .k(k), .st_pas(st_pas), .sb_pas(sb_pas),
    .st_drv(st_drv), .sb_drv(sb_drv),
    .alarm(alarm)
);

task checkAlarm(
    input kV, st_pasV, sb_pasV, st_drvV, sb_drvV,
    input alarmV
);
#1
k = kV; st_pas = st_pasV; sb_pas = sb_pasV;
st_drv = st_drvV; sb_drv = sb_drvV;
#1
assert(alarm == alarmV) else
    $fatal (1, "bad alarm, expected:%b got:%b", alarmV, alarm);
#1;
endtask

```

```

initial
begin
    k = 0; st_pas = 'b0; sb_pas = 'b0;
    st_drv = 'b0; sb_drv = 'h0;
    $monitor ("k:%b stPas:%b sbPas:%b stDrv:%b sbDrv:%b, a:%b",
        k, st_pas, sb_pas, st_drv, sb_drv, alarm);
    #10
    assert(alarm == 'h0) else $fatal(1, "bad alarm");
    #10
    checkAlarm(0,'b0,'h0, 'h0, 'h0, 'h0);

    for (int i = 0; i < 32; ++i) begin
        $display("i:%d [%b]", i, i[4:0]);
        if ( (i == 18) | (i == 22) | (i == 30)) // driver
            checkAlarm( i[4], i[3], i[2], i[1], i[0], 'h1);
        else if ( (i == 24 ) | (i == 25) | (i==27)) //passenger
            checkAlarm( i[4], i[3], i[2], i[1], i[0], 'h1);
        else if ( (i==26) )
            checkAlarm( i[4], i[3], i[2], i[1], i[0], 'h1);
        else
            checkAlarm( i[4], i[3], i[2], i[1], i[0], 'h0);
    end

    $display("@@@Passed");
end

endmodule

```

```

Vivado Simulator 2020.2
Time resolution is 1 ps
run -all
i:          0 [00000]
k:0 stPas:0 sbPas:0 stDrv:0 sbDrv:0, a:0
i:          1 [00001]
k:0 stPas:0 sbPas:0 stDrv:0 sbDrv:1, a:0
i:          2 [00010]
k:0 stPas:0 sbPas:0 stDrv:1 sbDrv:0, a:0
i:          3 [00011]
k:0 stPas:0 sbPas:0 stDrv:1 sbDrv:1, a:0
i:          4 [00100]
k:0 stPas:0 sbPas:1 stDrv:0 sbDrv:0, a:0
i:          5 [00101]

k:1 stPas:1 sbPas:1 stDrv:0 sbDrv:0, a:0
i:          29 [11101]
k:1 stPas:1 sbPas:1 stDrv:0 sbDrv:1, a:0
i:          30 [11110]
k:1 stPas:1 sbPas:1 stDrv:1 sbDrv:0, a:1
i:          31 [11111]
k:1 stPas:1 sbPas:1 stDrv:1 sbDrv:1, a:0
@@@Passed
exit

```

Launch with:

```

$ xvlog -sv TwoBeltAlarm_tb.sv
                TwoBeltAlarm.sv BeltAlarm.sv
$ xelab  tb -debug typical -s tb.snap
$ xsim tb.snap --R

```

03_Code Demo

'wire' vs 'logic'

- ***wire***

- Only used with 'assign' and module outputs
- Boolean combination of inputs
- Can never hold state

- ***logic***

- Used with 'always' and module outputs
- Can be Boolean combination of inputs
- Can hold state (but doesn't have to)

'wire' vs 'logic'

Verilog (OLD) Rules:

- Use **reg (or logic)** for left hand side (LHS) of signals assigned inside in **always** blocks
- Use Verilog **wire** for LHS of signals assigned outside **always** blocks

Much of the Internet still uses this!

This works for E210/B441!

'wire' vs 'logic'

SystemVerilog (NEW) Rules:

Just use 'logic'*

* **EXCEPT**

logic foo = `h42; **(BAD)**

wire foo = `h42; **(OK)**

logic foo;
foo = `h42; **(OK)**

'wire' vs 'logic'

SystemVerilog (NEW) Rules:

Just use 'logic'

<- Also works in E210/B441

* EXCEPT

```
logic foo = `h42; (BAD)
```

```
wire foo = `h42; (OK)
```

```
logic foo;  
assign foo = `h42; (OK)
```


Arrays in Verilog

- Bundle multiple wires together to form an array.

```
type [mostSignificantIndex:leastSignificantIndex] name;
```

- Examples

- `logic [15:0] x; //declare 16-bit array`
- `x[2] // access wire 2 within x`
- `x[5:2] //access wires 5 through 2`
- `x[5:2]= {1,0,y,z}; //concatenate 4 signals`

Arrays in Verilog

- Can also be used in module definitions

```
module multiply (  
    input    [7:0]    a,    //8-bit signal  
    input    [7:0]    b,    //8-bit signal  
    output   [15:0]    c     //16-bit signal  
);  
    //stuff  
endmodule
```

Arrays in Verilog

- Can also be used in module definitions

```
module multiply (  
    input    [7:0]    a,    //8-bit signal  
    input    [7:0]    b,    //8-bit signal  
    output logic [15:0] c    //16-bit signal  
);  
    //stuff  
endmodule
```

Can always add 'logic' when needed

Constants in Verilog

- A `logic` can only be a 1 or 0
- Arrays need more bits, how to specify?
- `8'h0 = 0000 0000 //using hex notation`
- `8'hff = 1111 1111`
- `8'b1 = 0000 0001 // using binary notation`
- `8'b10 = 0000 0010`
- `8'd8 = 0000 1000 //using decimal notation`

Constants in Verilog

```
logic      [7:0]  aa ;  
aa = {1'b0,1'b1,1'b0,1'b0,  
      1'b1,1'b0,1'b0,1'b0};  
aa = 8'b01001000;  
aa = {8{1'b1}}; //concat  
aa = 'hff; //inferred  
  
multiply m0(.a(aa), .b(8'h1), .c(cc));
```

always_comb Blocks

```
wire foo = x & y | z;
```

OLD Verilog

... is equivalent to ...

```
logic foo;  
assign foo = x & y | z;
```

New SystemVerilog

... is equivalent to ...

```
logic foo;  
always_comb //combinational  
    foo = x & y | z;
```

New SystemVerilog Syntax

always_comb adds if

```
module decoder (  
    input [1:0] sel,  
    output logic [3:0] out  
);  
always_comb begin  
    if (sel == 2'b00) begin  
        out = 4'b0001;  
    end else if (sel == 2'b01) begin  
        out = 4'b0010;  
    end else if (sel == 2'b10) begin  
        out = 4'b0100;  
    end else if (sel == 2'b11) begin  
        out = 4'b1000;  
    end  
end  
end  
endmodule
```

always_comb adds case

```
module decoder (  
    input [1:0] sel,  
    output logic [3:0] out  
);  
  
    always_comb begin  
        case(sel)  
            2'b00: out=4'b0001;  
            2'b01: out=4'b0010;  
            2'b10: out=4'b0100;  
            2'b11: out=4'b1000;  
        endcase  
    end  
  
endmodule
```


always_comb with case

```
module decoder (  
    input [1:0] sel,  
    output logic [3:0] out  
);  
  
    always_comb begin  
        case(sel)  
            2'b00: out=4'b0001;  
            2'b01: out=4'b0010;  
            2'b10: out=4'b0100;  
  
        endcase  
    end
```

// what about sel==2'b11?

```
endmodule
```

always_comb with case


```
module decoder (  
    input [1:0] sel,  
    output logic [3:0] out  
);  
  
always_comb begin  
    out = 4'b0000; //default  
    case(sel)  
        2'b00: out=4'b0001;  
        2'b01: out=4'b0010;  
        2'b10: out=4'b0100;  
        // what about sel==2'b11?  
    endcase  
end  
  
endmodule
```

Always specify
defaults for
always_comb!

Always specify defaults for
always_comb!

Always specify
defaults for
always_comb!

1-Bit “Full” Adder to ‘always_comb’

 


```
module FullAdder (
    input a,b,ci,
    output s, co
);

    assign s = a ^ b ^ ci;
    assign co = (a & b) |
                (( a ^ b) & ci);

endmodule
```

```
module Fu
endmodule
```

1-Bit “Full” Adder to ‘always_comb’

 

```
module FullAddr (  
    input a,b,ci,  
    output s, co  
);  
  
    assign s = a ^ b ^ ci;  
    assign co = (a & b) |  
                (( a ^ b) & ci);  
  
endmodule
```

```
module FullAddr (  
    input a,b,ci,  
    output logic s, co  
);  
  
    always_comb begin  
        s = a ^ b ^ ci;  
        co = (a & b) |  
              (( a ^ b) & ci);  
    end  
  
endmodule
```

Addition / Subtraction

Half Adder

$$\begin{array}{r} \text{X} + \text{y} = \text{carry} \quad \text{Sum} \\ \hline 0 \quad 0 \\ 0 \quad 1 \\ \hline 1 \quad 0 \\ \boxed{1 \quad 1} \end{array}$$

Binary Addition

- What if x and y are 2-bits each?



Full Adder

<u>X</u>	<u>y</u>	<u>C_{in}</u>	<u>C_{out} Sum</u>	
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

P2: use "+" in Verilog


Full Adder

i	x	y	z	C	S
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

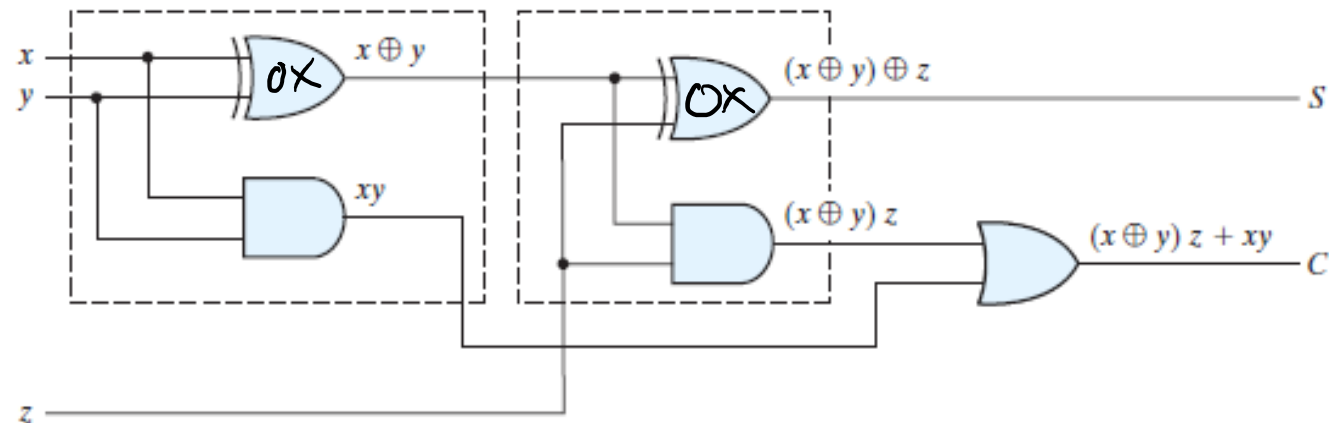 

$\log_{12} [7:0] \quad x = a + b;$

1-Bit “Full” Adder

 

```
module FullAddr (  
    input a,b,ci,  
    output s, co  
);  
  
    assign s = a ^ b ^ ci;  
    assign co = (a & b) | ((a ^ b) & ci);  
  
endmodule
```

Ripple-Carry Adder


$$\begin{array}{rcccc} & x_3 & x_2 & x_1 & x_0 \\ + & y_3 & y_2 & y_1 & y_0 \\ \hline z_4 & z_3 & z_2 & z_1 & z_0 \end{array}$$

Subtraction with Adders?

- We've done $A+B$, what about $A-B$?

Adder/Subtractor

 - Mode input:
 - If $M = 0$, then $S = A + B$, the circuit performs addition
 - If $M = 1$, then $S = A + \bar{B} + 1$, the circuit performs subtraction



Overflow

- Unsigned

$$\begin{array}{r} 10 \\ + 8 \\ \hline 18 \end{array}$$

- Signed

$$\begin{array}{r} 5 \\ + 6 \\ \hline 11 \end{array}$$

Overflow

$$\begin{array}{r} 10 \\ + 8 \\ \hline 18 \end{array}$$
$$\begin{array}{r} 1010 \\ + 1000 \\ \hline 10010 \end{array}$$

carry sum

unsigned = carry out bit
"overflow"

Signed

$$\begin{array}{r} 5 \\ + 6 \\ \hline 11 \end{array}$$

$$\begin{array}{r} 0101 \\ 0110 \\ \hline \end{array}$$

$$\boxed{0101}^{\text{signed}}$$

carry = 0 \Rightarrow No overflow?

$$5 = 0101 \quad 1010 \rightarrow 1011$$
$$6 = 0110$$

$$= -(0100 + 1) = -(0101) = -5 \leftarrow \text{overflow!}$$

Overflow for signed numbers?

$$\begin{array}{r} -2 \\ + -1 \\ \hline -3 \end{array}$$

$$\begin{array}{r} -7 \\ + -7 \\ \hline -14 \end{array}$$

Overflow for signed numbers?

$$\begin{array}{r} -2 \\ + -1 \\ \hline \end{array} \quad \begin{array}{l} -(0010) = 1101 + 1 = \boxed{1}110 \\ -(0001) = 1110 + 1 = \underline{+1111} \\ 10001 \end{array}$$

Carry is same \Rightarrow no overflow

$$\begin{array}{r} +2 \\ + -1 \\ \hline \end{array} \quad \begin{array}{l} (1110) = 0010 \\ = +1111 \\ \underline{} 10001 \end{array}$$

Carry is same \Rightarrow no overflow

$$\begin{array}{r}
 -7 \\
 + -7 \\
 \hline
 \end{array}
 \quad
 \begin{array}{l}
 -(0111) = 1000+1 = 1001 \\
 -(0111) = 1000+1 = +1001 \\
 \hline
 10010
 \end{array}$$

(1001) → carry is different
 ⇒ overflow

$$\begin{array}{r}
 +7 \\
 + +7 \\
 \hline
 \end{array}
 \quad
 \begin{array}{l}
 0111 \\
 0111 \\
 + 0111 \\
 \hline
 01110
 \end{array}$$

(0111) → carry is different
 ⇒ overflow

Overflow for signed numbers

$$\begin{array}{rcccc} & & X & X & X & X \\ + & 0 & 0 & 0 & 0 & \\ \hline 1 & 1 & 1 & 1 & 1 & \end{array}$$


Overflow detection

- When two numbers with n digits each are added and the sum is a number occupying $n + 1$ digits, we say that an overflow occurred.
- The detection of an overflow after the addition of two binary numbers depends on whether the numbers are considered to be signed or unsigned.
- When two unsigned numbers are added, an overflow is detected from the end carry out of the most significant position.
- In case of signed numbers, two details are important:
 - the leftmost bit always represents the sign,
 - negative numbers are in 2's-complement form.
- When two signed numbers are added:
 - the sign bit is treated as part of the number
 - the end carry does not indicate an overflow.

Overflow detection

- An overflow cannot occur after an addition if one number is positive and the other is negative, since adding a positive number to a negative number produces a result whose magnitude is smaller than the larger of the two original numbers.
- An overflow may occur if the two numbers added are both positive or both negative.
- An overflow condition can be detected by observing the carry into the sign bit position and the carry out of the sign bit position.
 - If these two carries are equal, there was no overflow.
 - If these two carries are not equal, an overflow has occurred.
- If the two carries are applied to an exclusive-OR gate, an overflow is detected when the output of the gate is equal to 1.

Adder with overflow detection

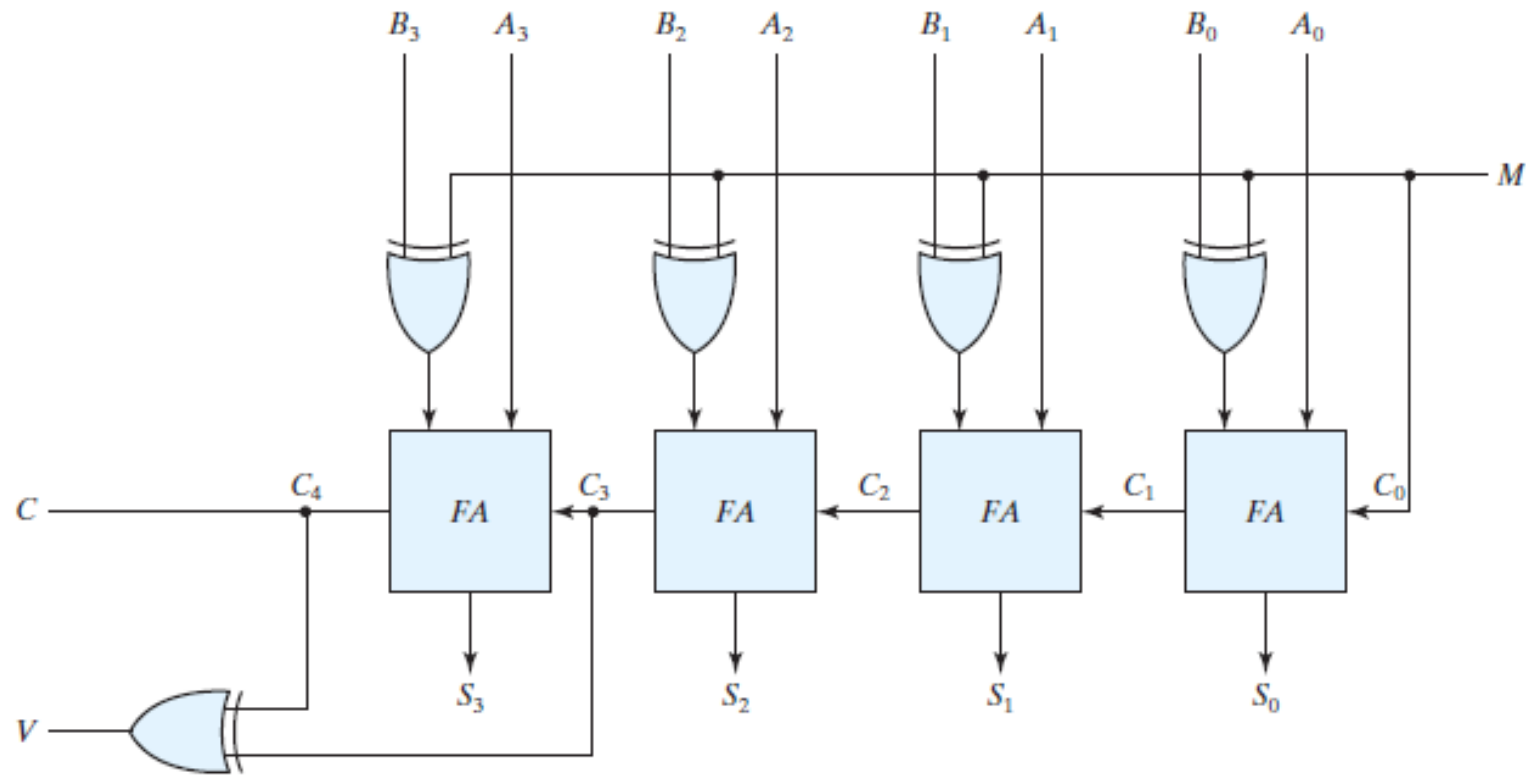

P3 Tips

Next Time


- Latches / Flip-Flops

Gate Delay

- Gates are not magic, they are physical
- Takes time for changes flow through
- Assume 5ps (5E-12) / gate
- How fast can we update our adder?

Full Adder Gate Delay


- Assume 5ps/gate

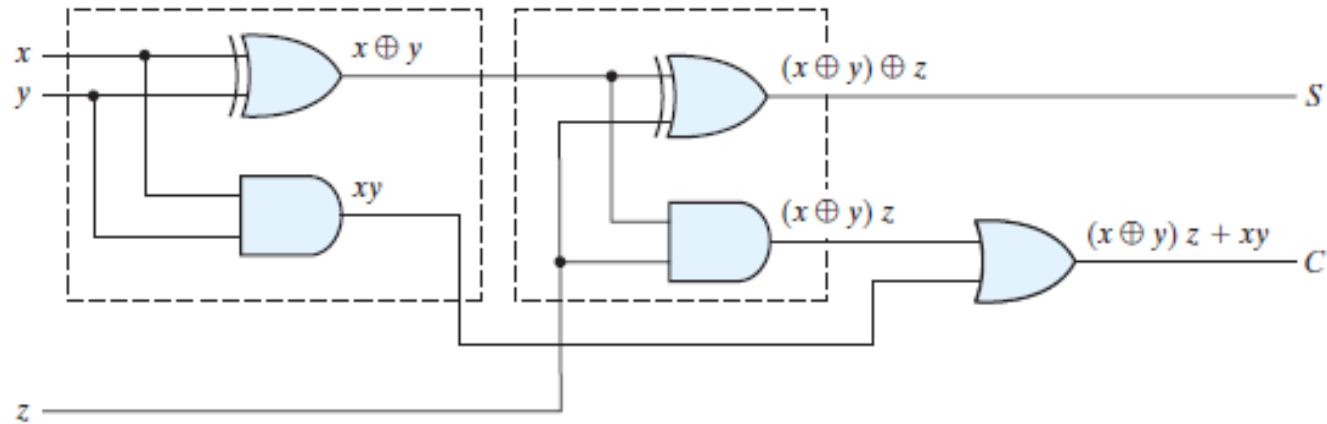

- What is the total delay on s ? on c ?

Ripple-Carry Gate Delays

- What is the total delay here?

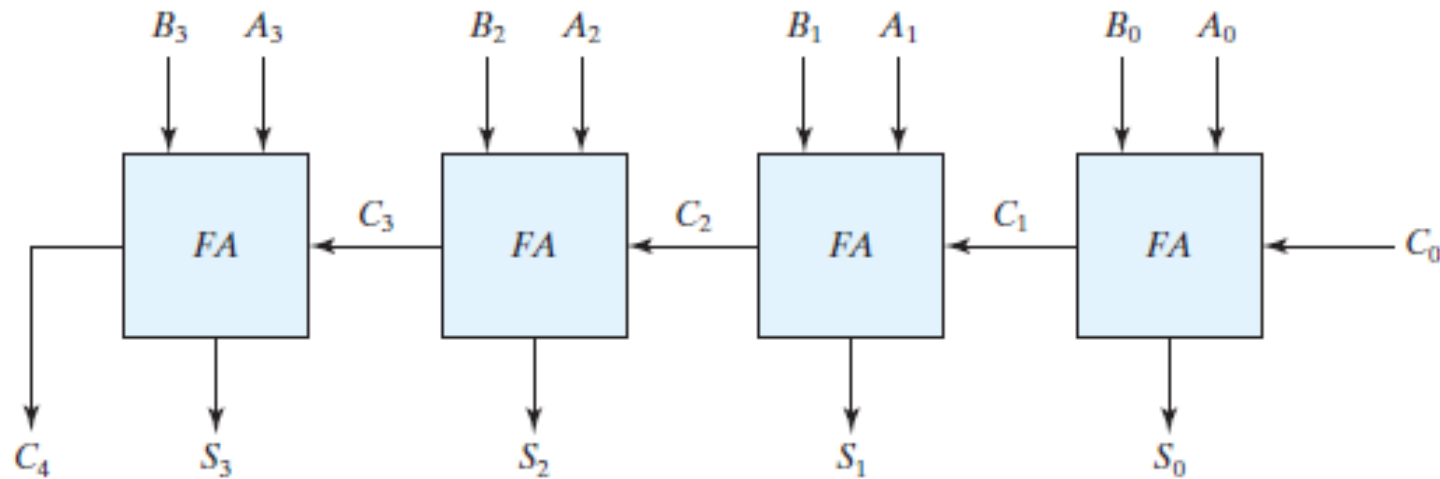

Adder Gate Delays

- What is the total delay for:
 - 1-bit addition:
 - 4-bit addition:
 - 8-bit addition:
 - 16-bit addition:
 - 32-bit addition:
 - 64-bit addition:

Adder Gate Delays

- What is the total delay for:

- 1-bit addition:
- 4-bit addition:
- 8-bit addition:
- 16-bit addition:
- 32-bit addition:
- 64-bit addition:

15 ps

60 ps

120 ps

240 ps

480 ps

960 ps = ≈ 1 GHz

Faster Adder Options?

- What can be done to build a faster 64-bit adder?

Next Time

- Latches / Flip-Flops