

ENGR 210 / CSCI B441
“Digital Design”

SPI I

Andrew Lukefahr

Announcements

- P8 – Elevator Controller is out

- This one is hard.

due Friday

- P9 – SPI is out → Last one 😊

- This one is new. Might be some changes.

- The end is in sight...

P9 SPI QuickStart

- We build the Vivado project for you:

```
git clone https://github.com/ENGR210/P9\_SPI.git  
cd P9_SPI  
make setup  
vivado vivado/vivado.xpr
```


- We provide you with Testbenches
- Same ones as the Autograder!

Always specify
defaults for
always_comb!


BLOCKING (=) FOR
always_comb

NON-BLOCKING (<=) for
always_ff

Glitch

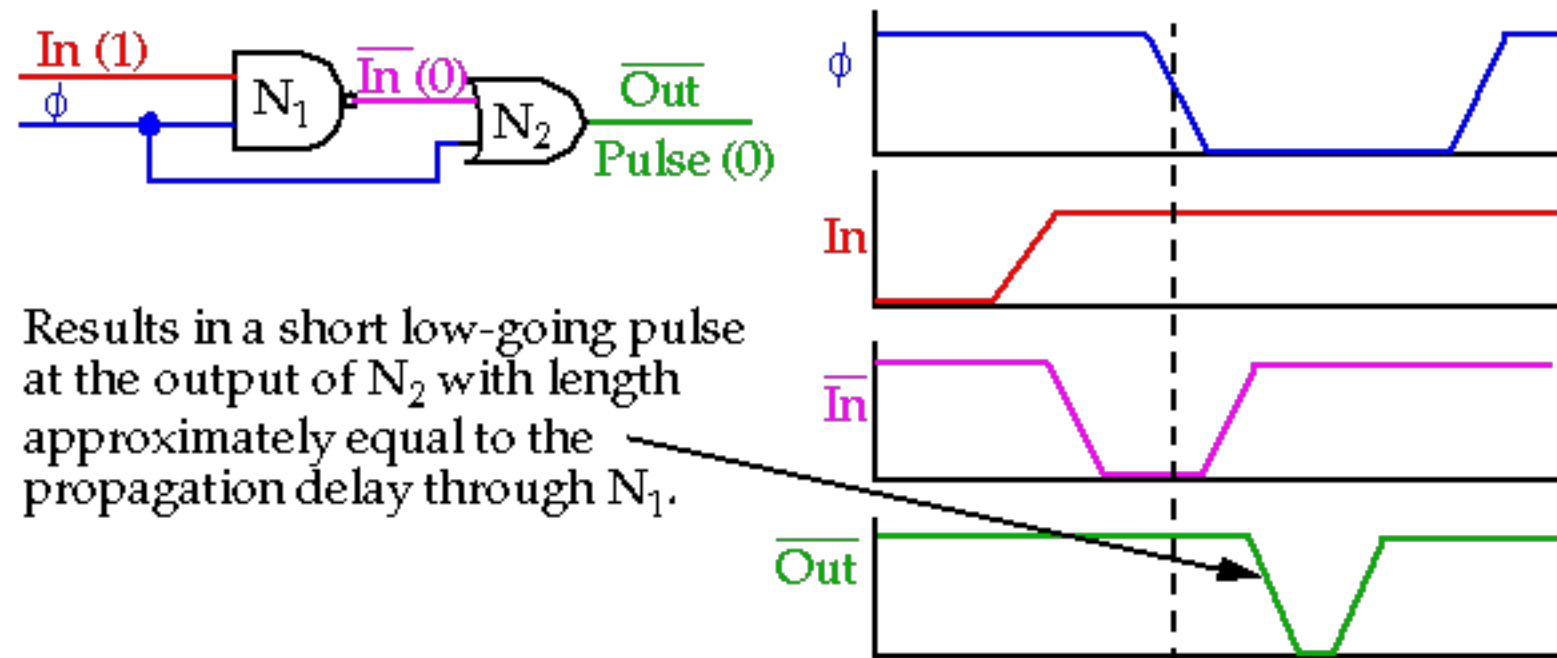


Setup/Hold Time

 

Slack

- Extra time between combinational propagation delay and setup time
- Time between stable input to Flip-Flop and next clock edge

 - Vivado:
 - WNS: Worst-case Negative Slack



- If this number is <0 , your circuit will (probably) not work

Correct for (; ;) Loops in Verilog

This Code:



```
integer x; //or genvar x
for (x = 0; x < 4; x++) begin
    assign y[x] = a[x+right];
end
```

Expands to:


```
assign y[0] = a[0 + right];
assign y[1] = a[1 + right];
assign y[2] = a[2 + right];
assign y[3] = a[3 + right];
```

Converts serial input to parallel output

Shift Register

 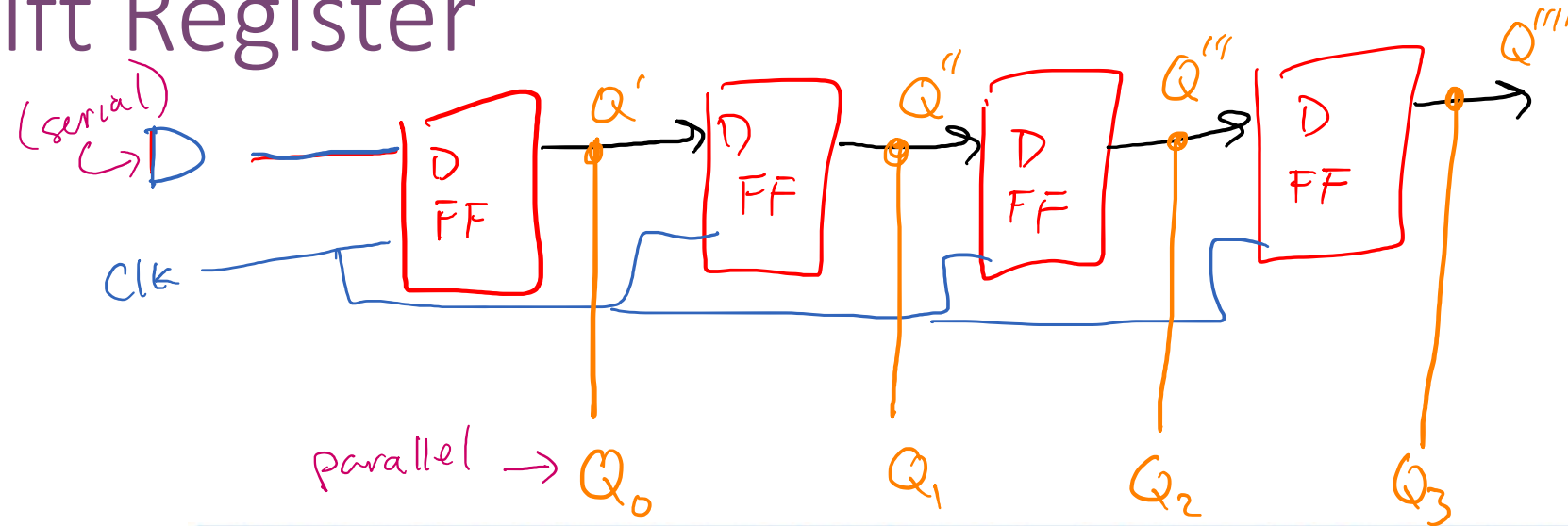


What about this circuit?

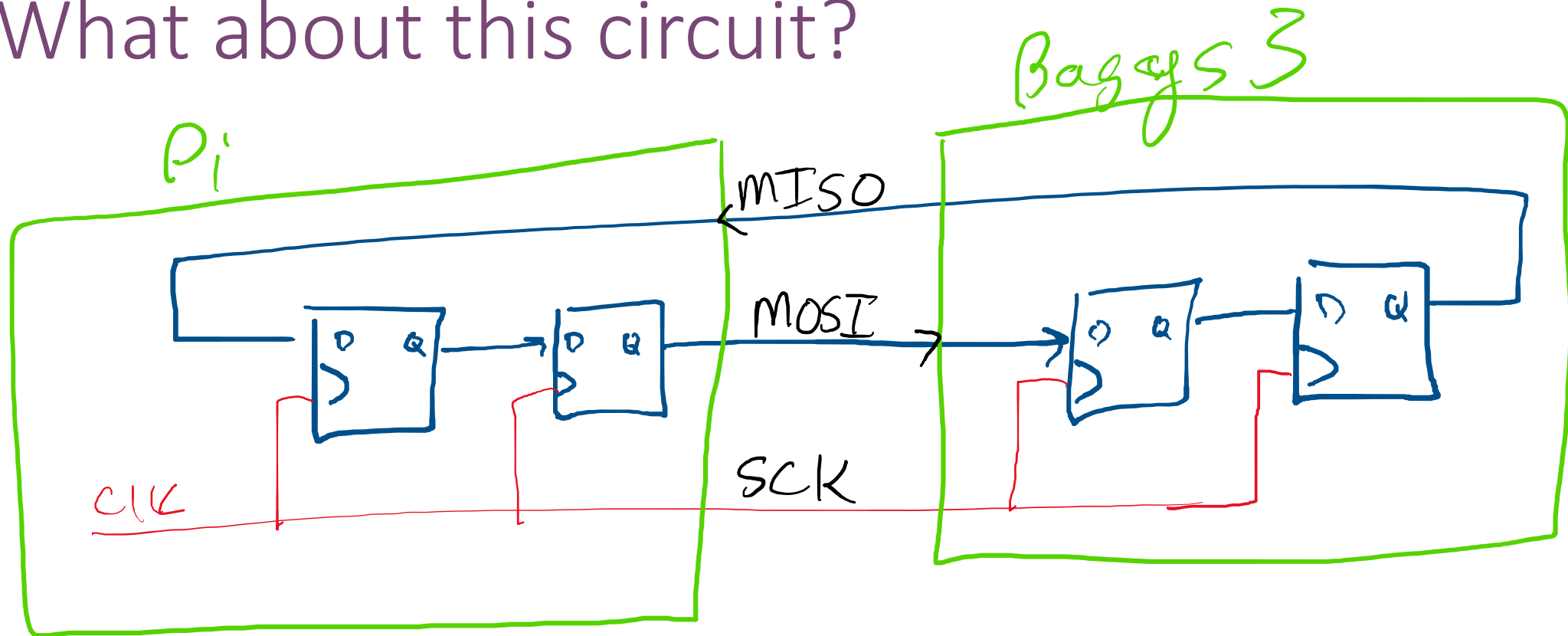

MOSI: Master Out Slave In
Serial Data Out (SDO)


MISO: Master In Slave Out
Serial Data In (SDI)

SPI

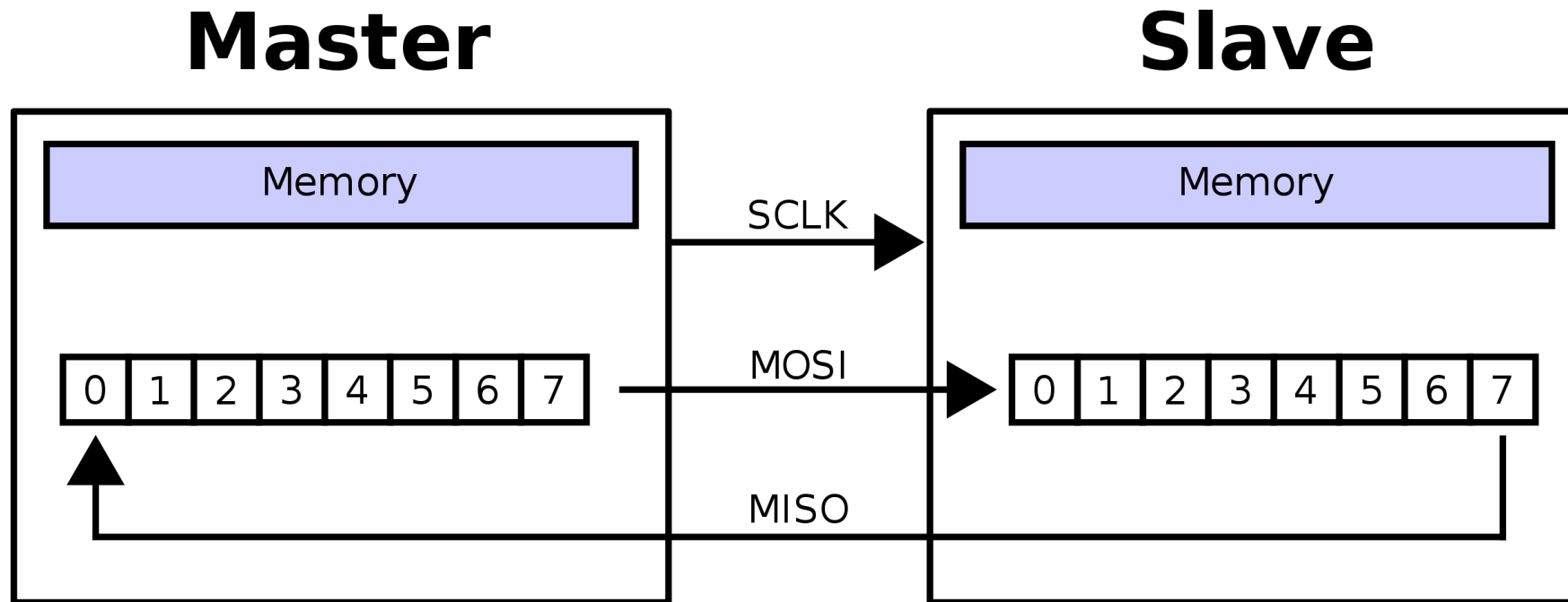

When to CAPTURE new data?

Rising Edge of SCK!

 


When to SEND new data?





② falling
SCK

edge of
~~CLOCK~~
SCK



~~DATA~~
MISO

 



Clocks on Slave SPI

  


Clocks on Slave SPI

  


Clocks on Slave SPI

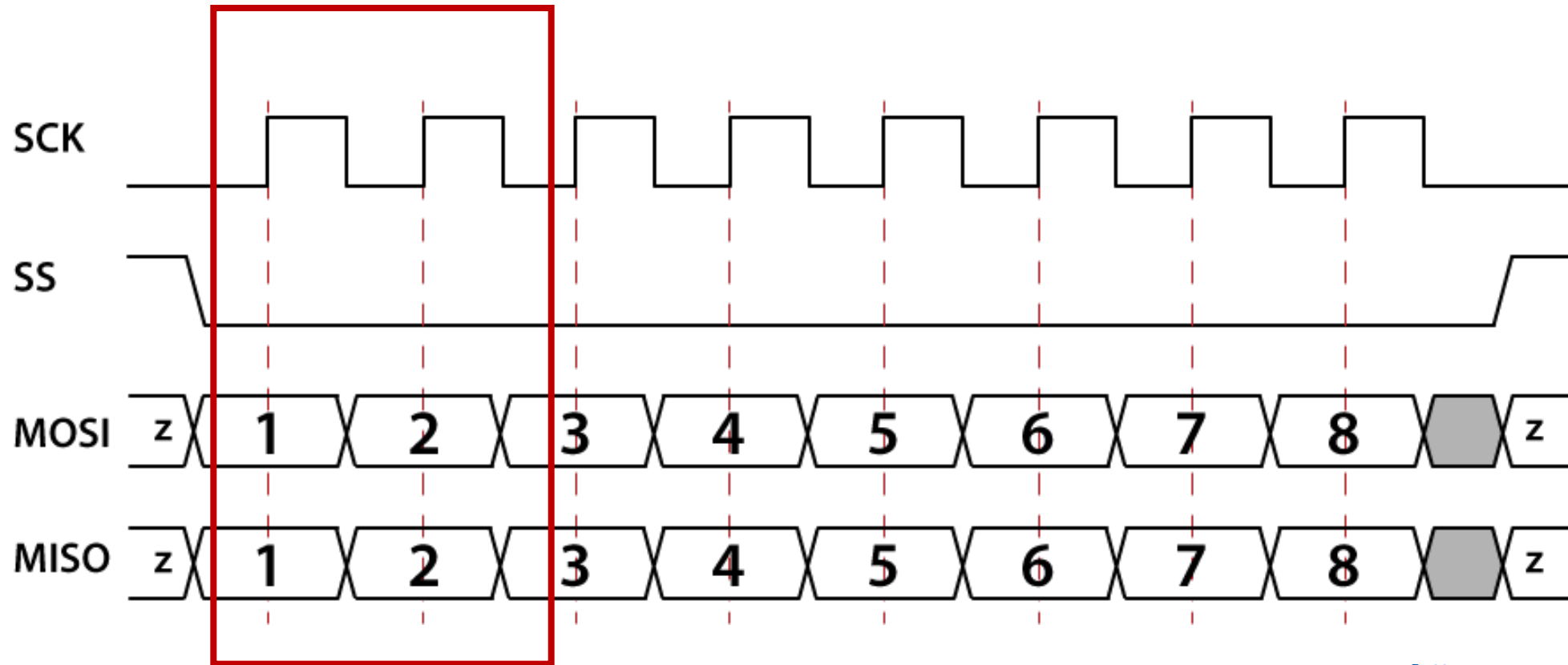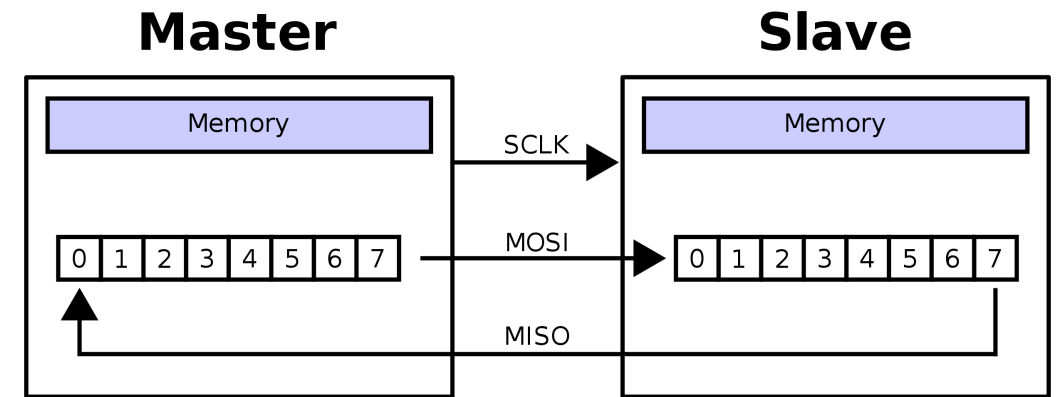


Clocks on Slave SPI

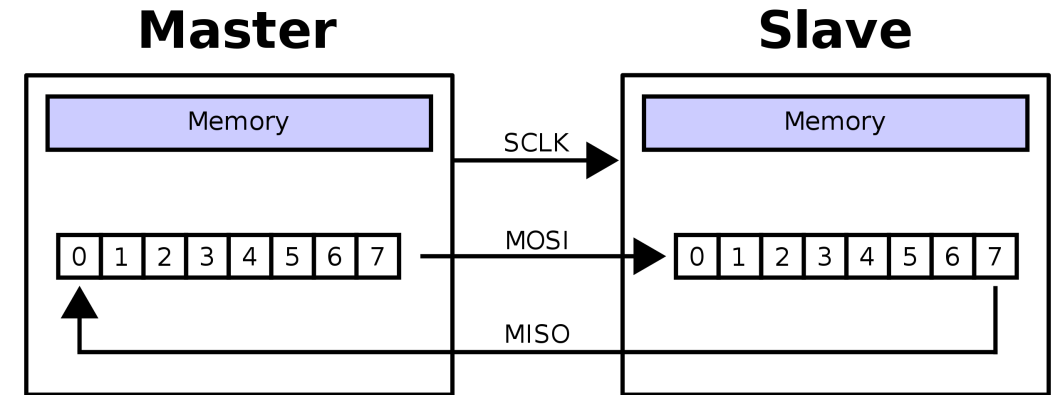


CLK100MHz

 

Finding SCLK Edges

 


Finding SCLK Edges

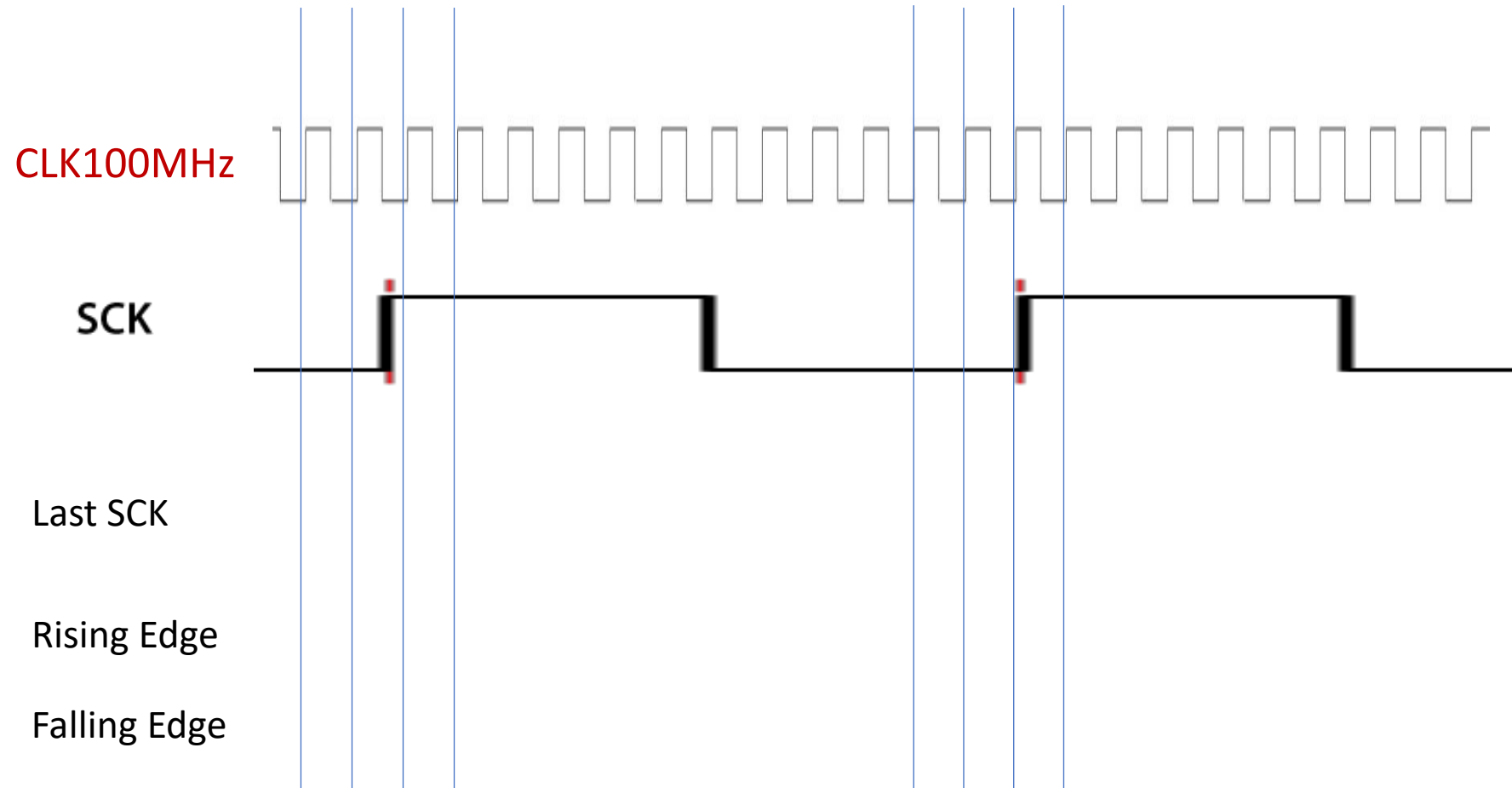


How to capture MOSI?

Not 100% right yet!

 


When to send MISO?

 


How to send MISO?


Not 100% right yet!

 


Timing Issues?

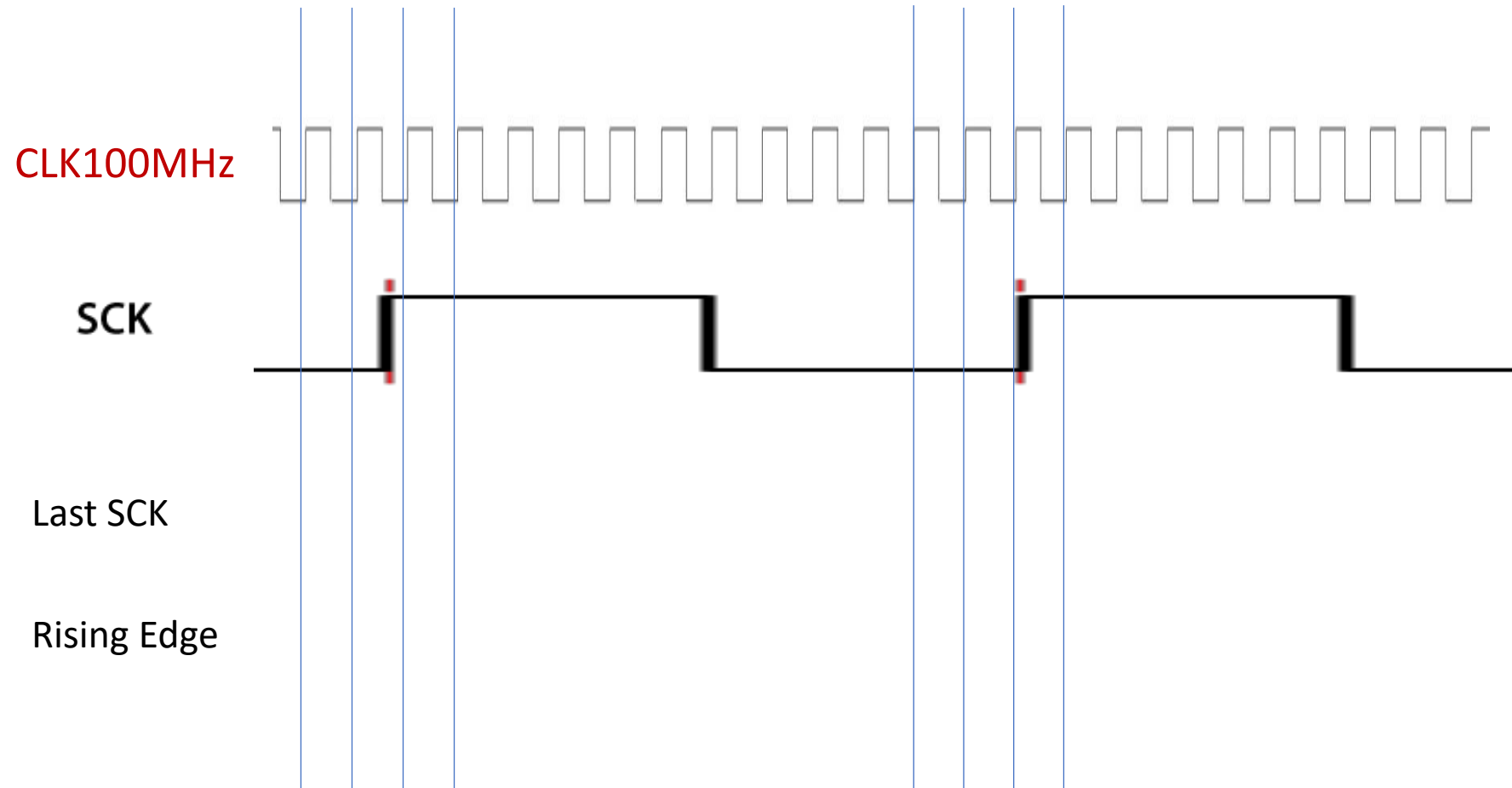

Timing Issues

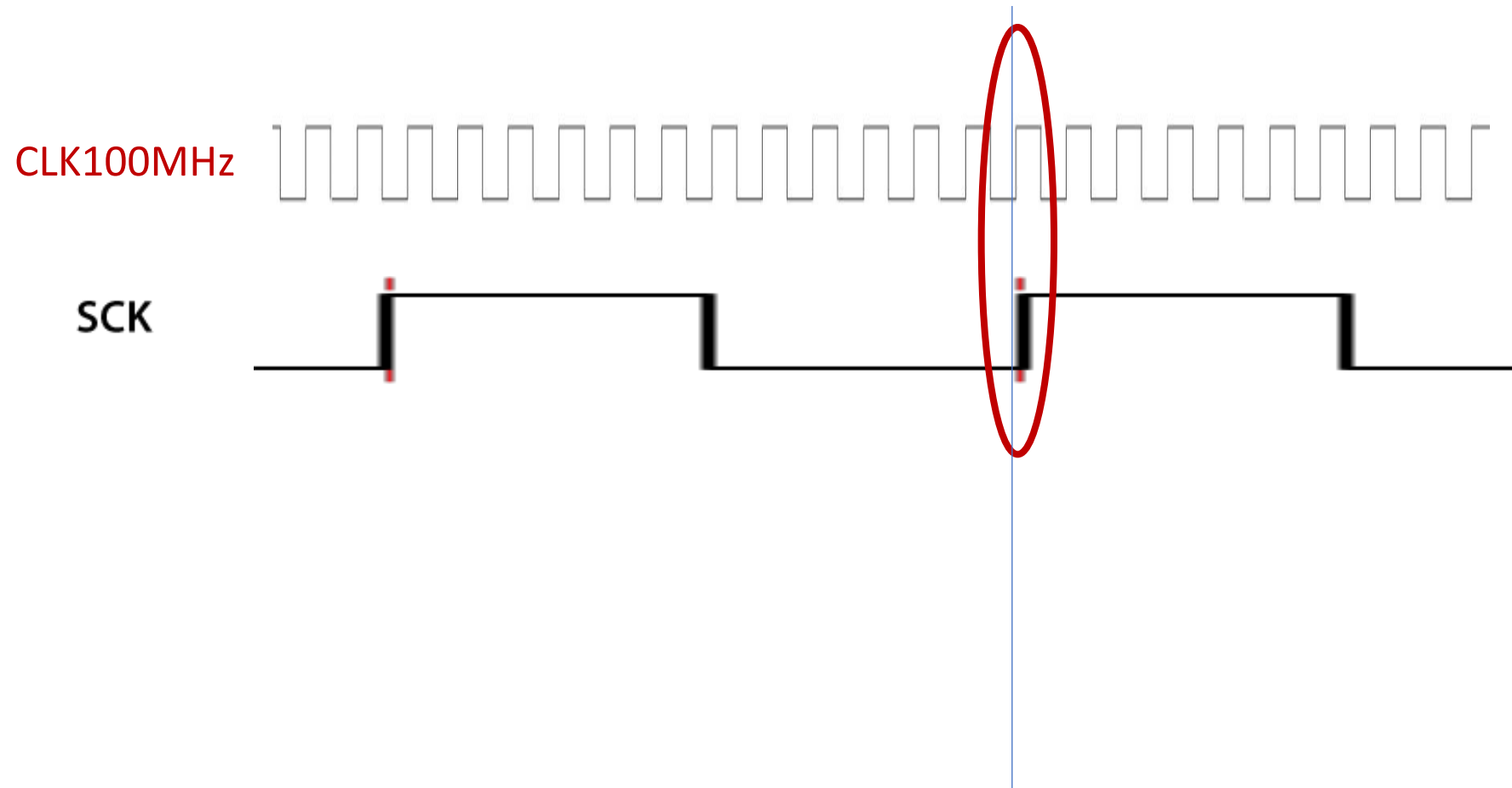

Setup/Hold Time


 


Next Time



- Synchronizers
- Tri-State Logic
- MMIO

Why Synchronizers?

Synchronizers

  

What about 'Z'?

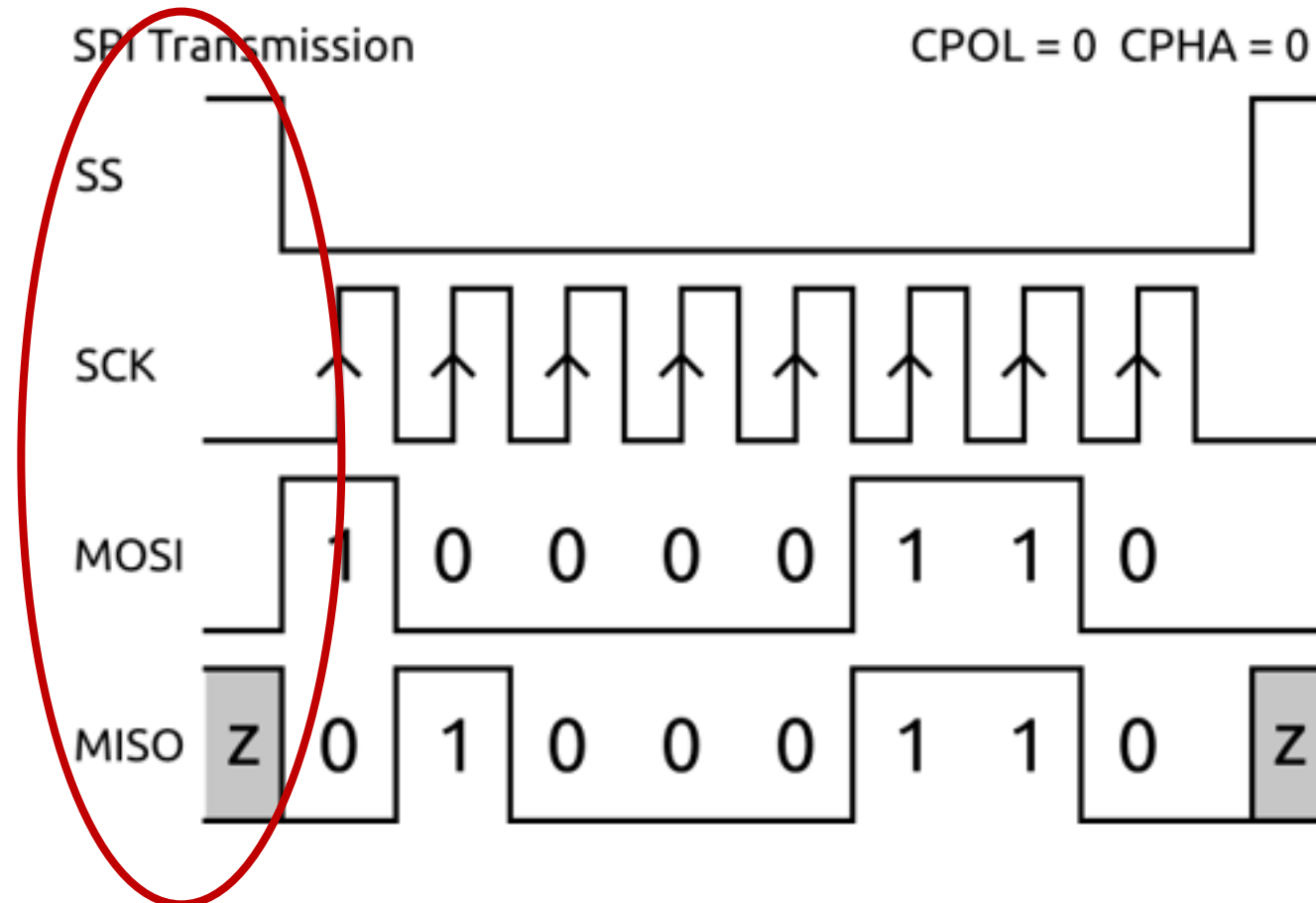 


What is 'Z'?

- Z: High Impedance
 - Stop driving a logical value
 - Pretend I'm not connected
- “Tri-State” signals:
 - 1: this is logical true
 - 0: this is logical false
 - X: The simulation tools don't know if it's 1 or 0
 - Z: this is “high impedance”

Tri-State Logic

Problems with Tri-State Logic

- What if two signals “drive” at once?

 

Solution: Don't Do That!

NEVER DO THAT!